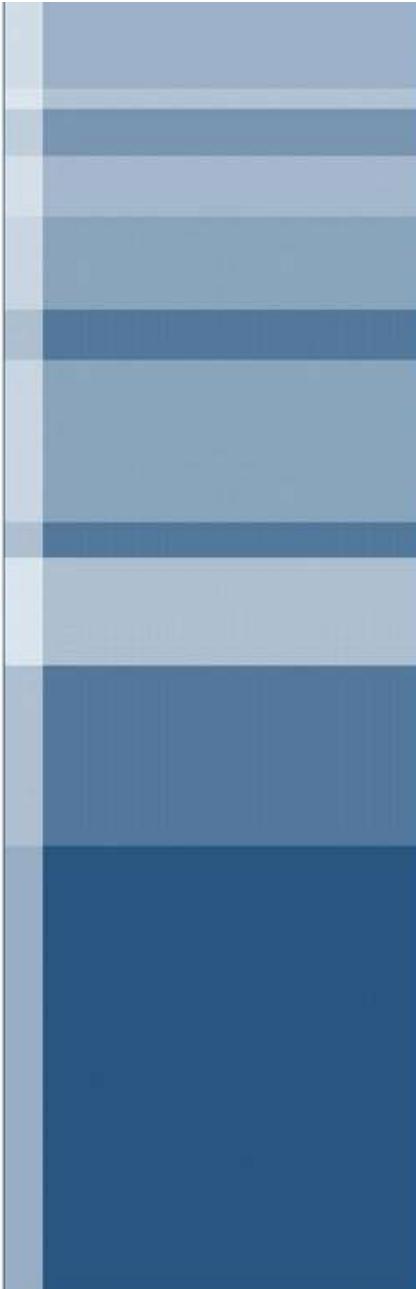




DIPARTIMENTO DI ELETTRONICA,  
INFORMAZIONE E BIOINGEGNERIA



# Power Electronics

Part 8

Massimo Ghioni




# Isolated DC-DC converters

# What is isolation?
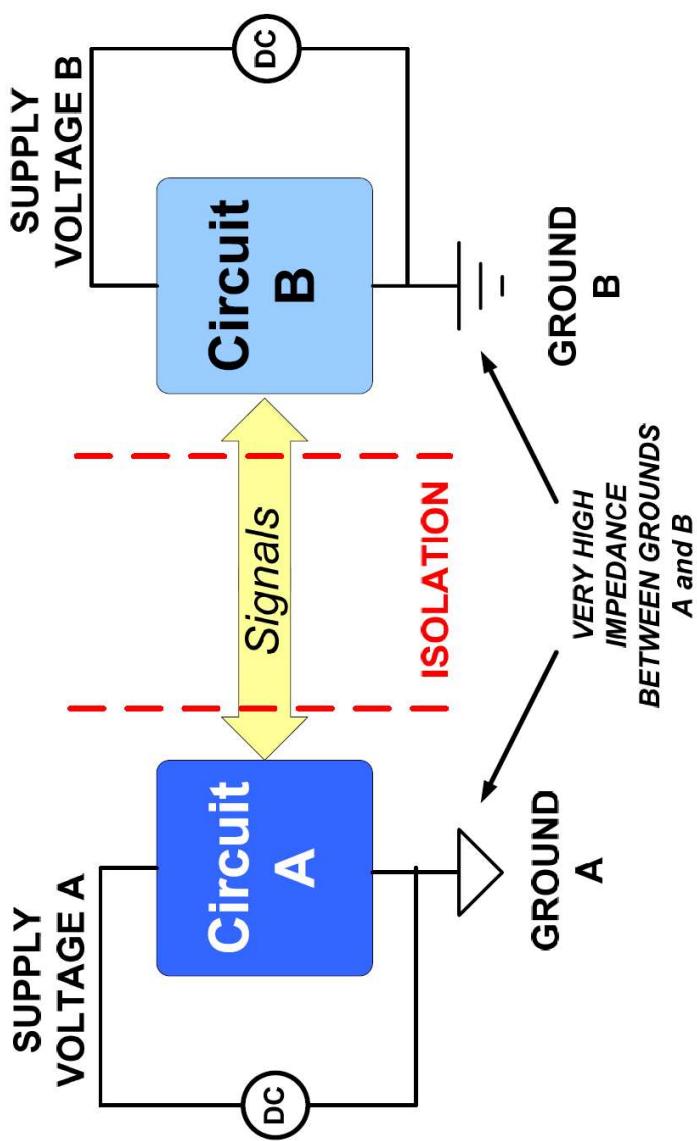
## Galvanic isolation


- No current flow from one circuit to another
- Signal information passes from one circuit to another



# Isolated DC-DC converters
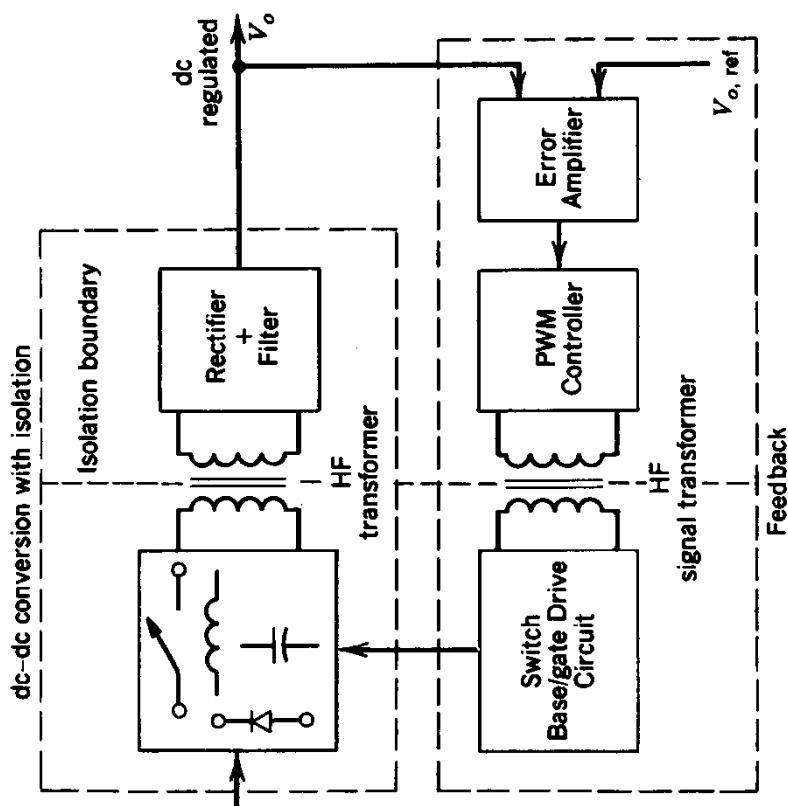
## Objectives

- Isolation of input and output ground connections, to meet safety requirements
- Minimization of current and voltage stresses when a large step-up or step-down conversion ratio is needed → use transformer turns ratio
  - Obtain multiple output voltages via multiple transformer secondary windings and multiple converter secondary circuits



Note: this is only one possible arrangement. Controller often on primary side with switch.

- Reduction of transformer size by incorporating high frequency isolation transformer inside converter

# Multiple outputs

- Transformer allows multiple outputs to be “quasi-regulated” using a single controller and feedback loop.
- e.g. most PC power supplies achieve multiple outputs this way.


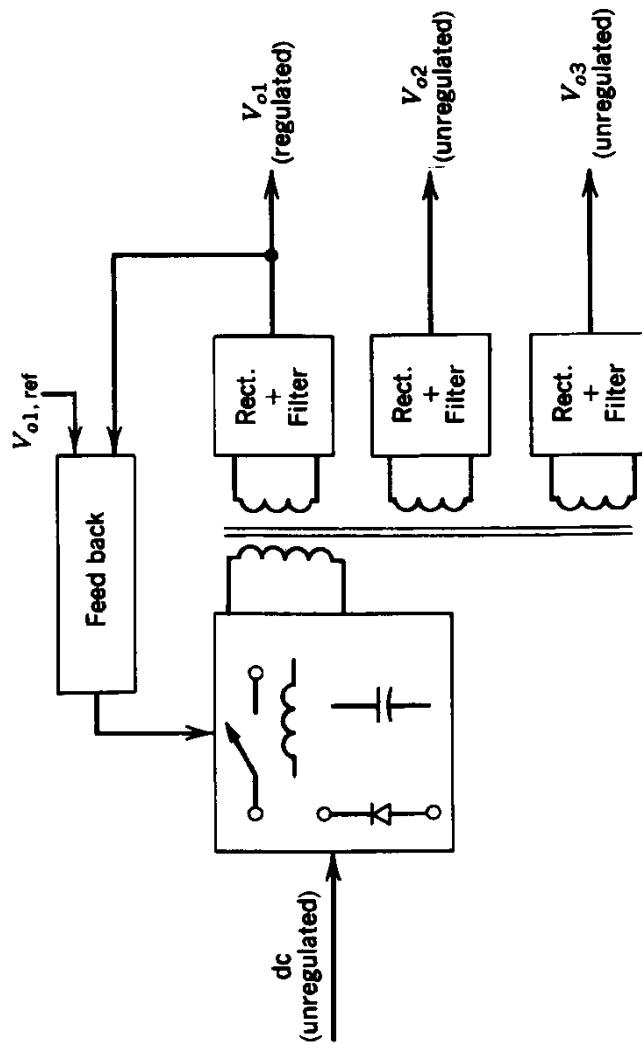


Figure 10-3 Multiple outputs.

- In practice, feedback loop uses a “weighted average” of output voltages to achieve best overall regulation.
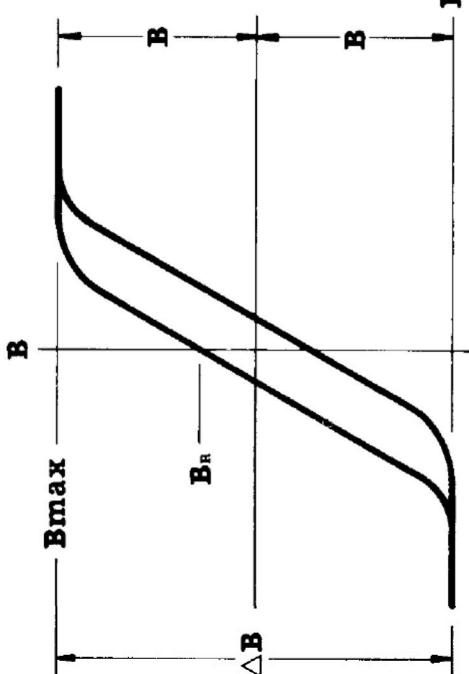
# Transformer core size

The power handling capacity of a transformer core can be determined by its  $WaAc$  product, where  $Wa$  is the available core window area, and  $Ac$  is the effective core cross-sectional area.



The  $WaAc$ /power-output relationship is obtained by starting with Faraday's Law:

$$E = 4B Ac Nf \times 10^{-8} \text{ (square wave)} \quad (1)$$

$$E = 4.44 BaC Nf \times 10^{-8} \text{ (sine wave)} \quad (1a)$$

Where:

$E$  = applied voltage (rms)

$B$  = flux density in gauss

$Ac$  = core area in  $\text{cm}^2$

$N$  = number of turns

$f$  = frequency in Hz

$Aw$  = wire area in  $\text{cm}^2$

$Wa$  = window area in  $\text{cm}^2$ :

core window for toroids  
bobbin window for other cores

$C$  = current capacity in  $\text{cm}^2/\text{amp}$

Solving (1) for  $NaC$

$$NaC = \frac{E \times 10^8}{4Bf} \quad (2)$$

$$K = \frac{NaW}{Wa} \quad \text{thus } N = \frac{KWa}{Aw} \quad \text{and } NaC = \frac{KWaAc}{Aw} \quad (3)$$

Combining (2) and (3) and solving for  $WaAc$ :

$$WaAc = \frac{E Aw \times 10^8}{4B f K}, \text{ where } WaAc = \text{cm}^4 \quad (4)$$

In addition:

$$C = Aw/l \quad \text{or} \quad Aw = lC \quad e = P_o/P_i \quad P_i = E|$$

Thus:

$$E Aw = E|C = P_i C = P_o C/e$$

Substituting for  $E Aw$  in (4), we obtain:

$$WaAc = \frac{P_o C \times 10^8}{4eB f K} \quad (5)$$

# Transformer modeling


7

Two windings, no air gap:

$$\mathcal{R} = \frac{\ell_m}{\mu A_c}$$


$$\mathcal{F}_c = n_1 i_1 + n_2 i_2$$

$$\Phi \mathcal{R} = n_1 i_1 + n_2 i_2$$

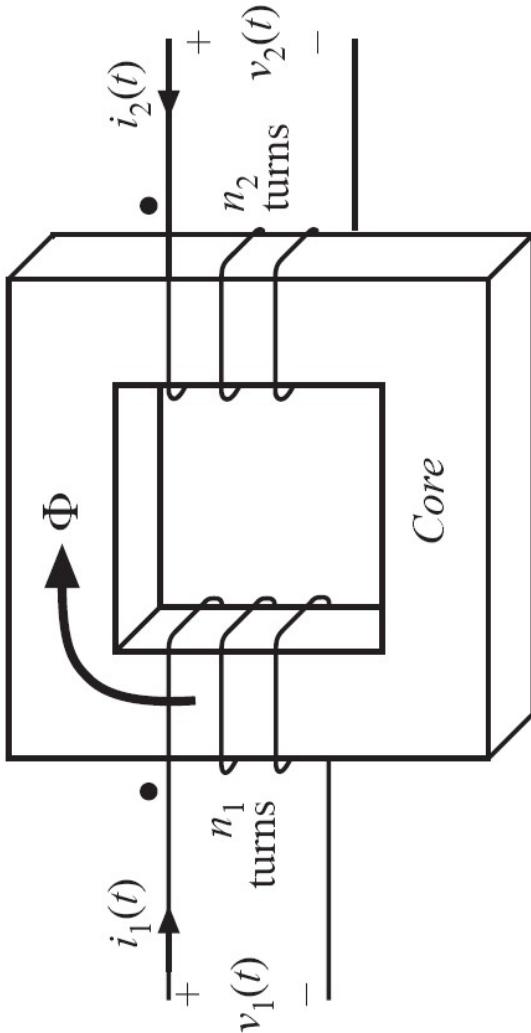
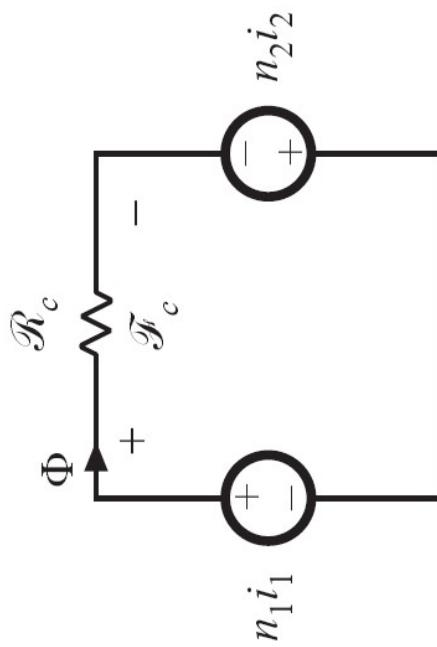
## Dot convention

The primary and secondary currents flowing into the winding terminals marked • produce a mutually additive magnetic flux.



Magnetic circuit model:

# The ideal transformer

In the ideal transformer, the core reluctance  $\mathcal{R}_c$  approaches zero.

MMF  $\mathcal{F}_c = \Phi \mathcal{R}_c$  also approaches zero. We then obtain

$$0 = n_1 i_1 + n_2 i_2$$

Also, by Faraday's law,



$$\begin{aligned} v_1 &= n_1 \frac{d\Phi}{dt} \\ v_2 &= n_2 \frac{d\Phi}{dt} \end{aligned}$$

Eliminate  $\Phi$ :

$$\frac{d\Phi}{dt} = \frac{v_1}{n_1} = \frac{v_2}{n_2}$$

Ideal transformer equations:
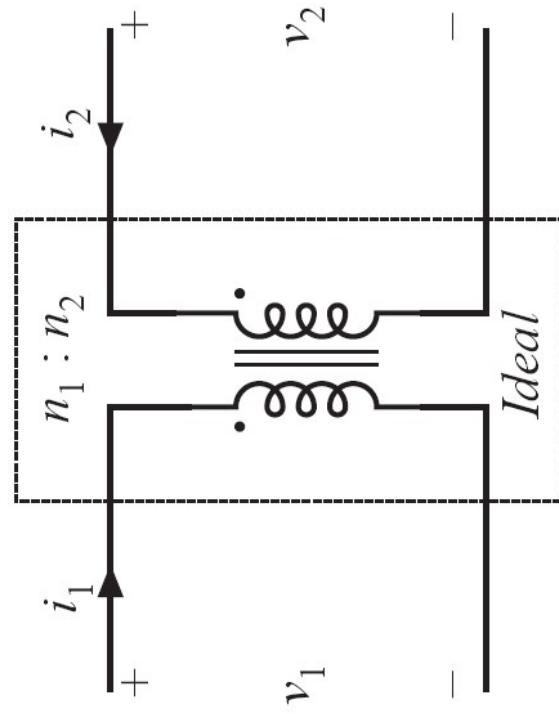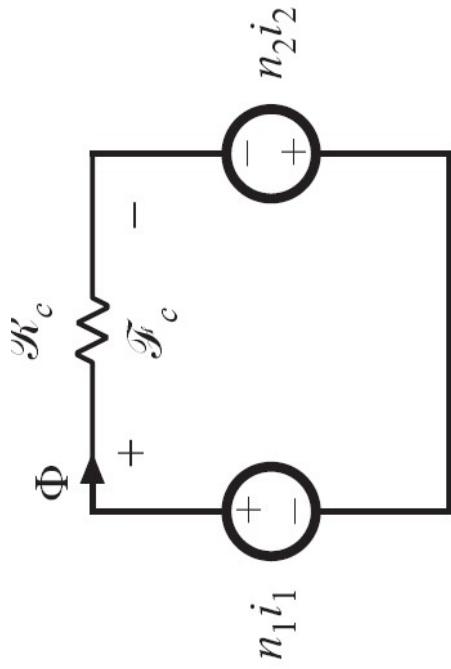
$$\frac{v_1}{n_1} = \frac{v_2}{n_2} \quad \text{and} \quad n_1 i_1 + n_2 i_2 = 0$$



# The magnetizing inductance


9

For nonzero core reluctance, we obtain

$$\Phi \mathcal{R} = n_1 i_1 + n_2 i_2 \quad \text{with} \quad v_1 = n_1 \frac{d\Phi}{dt}$$

Eliminate  $\Phi$ :
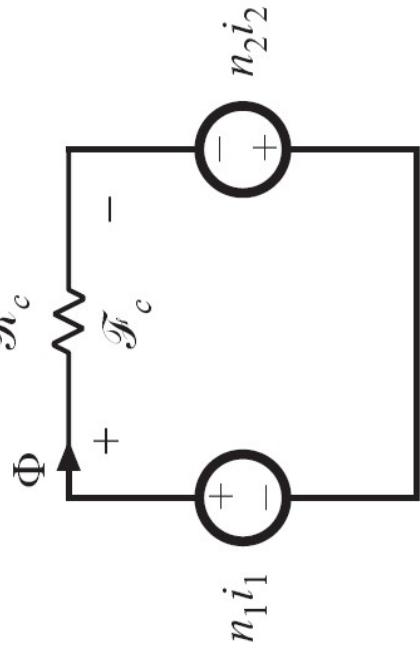
$$v_1 = \frac{n_1^2}{\mathcal{R}} \frac{d}{dt} \left[ i_1 + \frac{n_2}{n_1} i_2 \right]$$




This equation is of the form

$$v_1 = L_M \frac{di_M}{dt}$$

with

$$L_M = \frac{n_1^2}{\mathcal{R}}$$

$$i_M = i_1 + \frac{n_2}{n_1} i_2$$

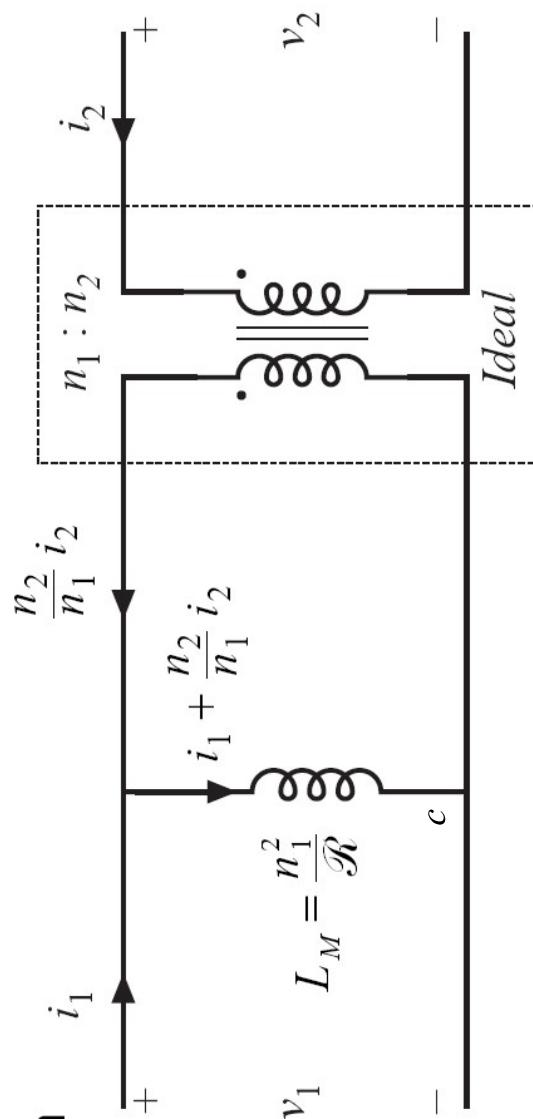


Magnetizing current  $i_m(t)$ : the current required to create  $H_c(t)$  that couples primary and secondary windings through magnetic induction.

# The magnetizing inductance (cont'd)

- Models magnetization of core material
- A real, physical inductor, that exhibits saturation and hysteresis
- If the secondary winding is disconnected:
  - we are left with the primary winding on the core
  - primary winding then behaves as an inductor
  - the resulting inductor is the magnetizing inductance, referred to the primary winding
- Magnetizing current causes the ratio of winding currents to differ from the turns ratio

# Add leakage fluxes

11

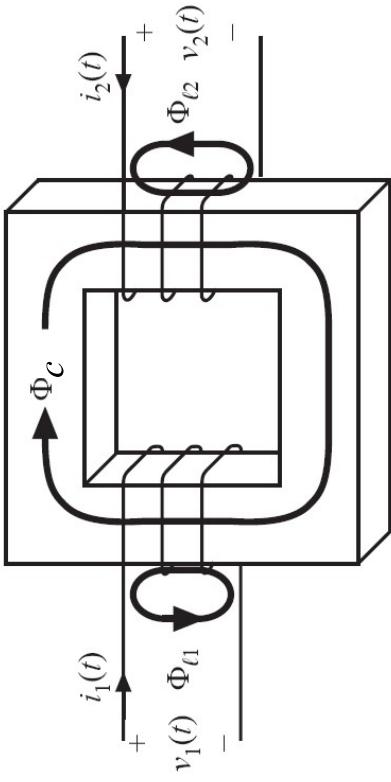

$$\phi_c = \frac{N_1 i_1 + N_2 i_2}{\mathcal{R}_c}; \quad \phi_{l1} = \frac{N_1 i_1}{\mathcal{R}_{l1}}; \quad \phi_{l2} = \frac{N_2 i_2}{\mathcal{R}_{l2}}$$

$$\lambda_1 = N_1 (\phi_c + \phi_{l1}); \quad \lambda_2 = N_2 (\phi_c + \phi_{l2})$$

$$(1)$$

$$v_1 = \frac{d\lambda_1}{dt} = L_{l1} \frac{di_1}{dt} + L_m \left( \frac{di_1}{dt} + \frac{N_2}{N_1} \frac{di_2}{dt} \right)$$

$$(2)$$


$$v_2 = \frac{d\lambda_2}{dt} = L_{l2} \frac{di_2}{dt} + \frac{N_2}{N_1} L_m \left( \frac{di_1}{dt} + \frac{N_2}{N_1} \frac{di_2}{dt} \right)$$

with

$$L_m = \frac{N_1^2}{\mathcal{R}_c}; \quad L_{l1} = \frac{N_1^2}{\mathcal{R}_{l1}}; \quad L_{l2} = \frac{N_2^2}{\mathcal{R}_{l2}}$$

- Equations (1) and (2) provide a mathematical description of the input-output characteristics of a generic transformer



# Leakage inductances

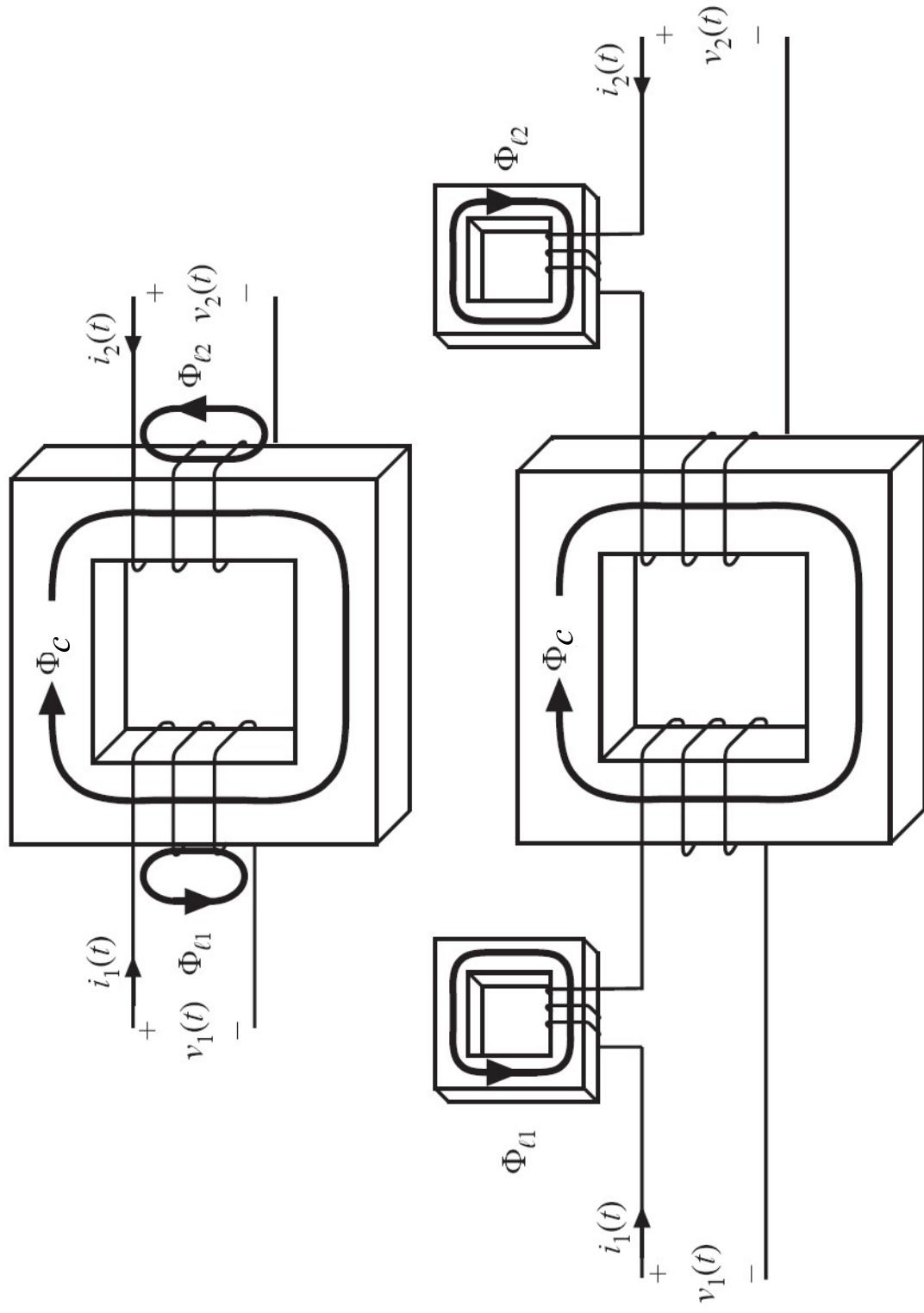
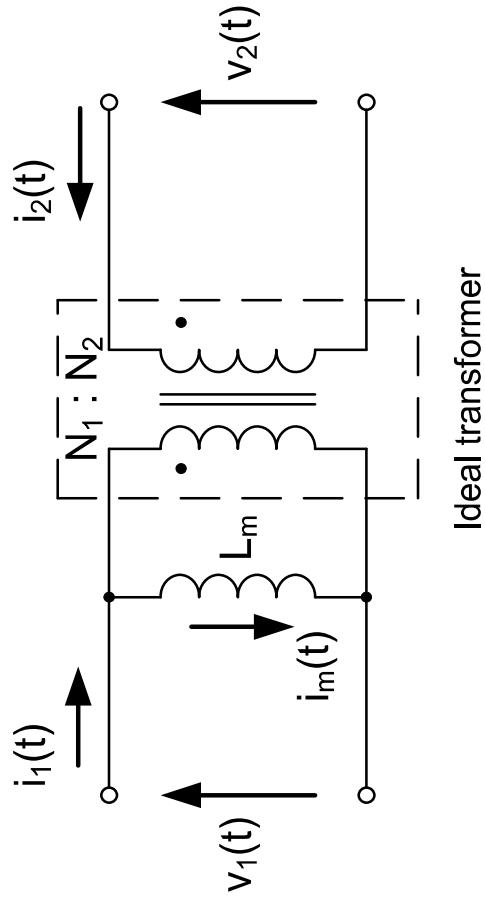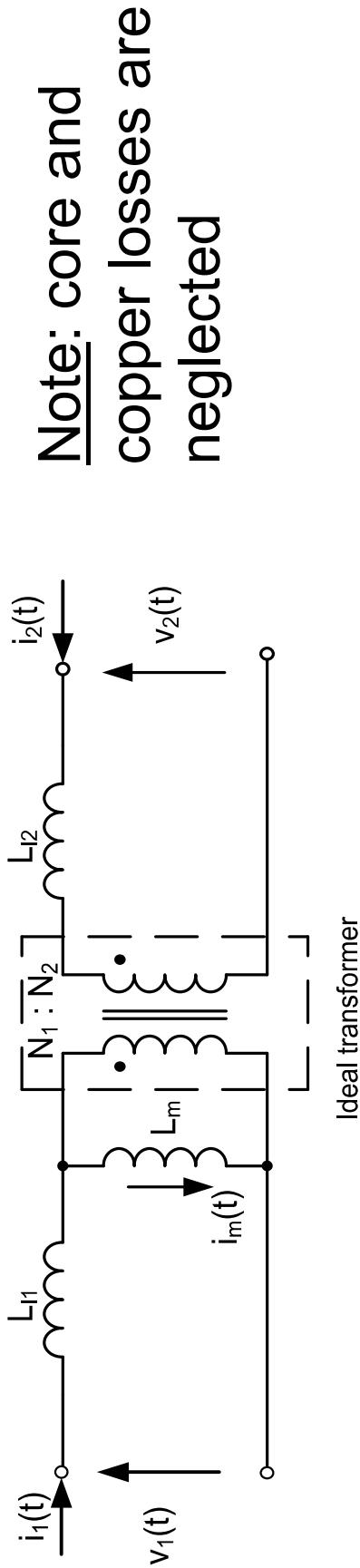
# Transformer model ( $\pi$ - model)


13

An equivalent model that satisfies Eqs. (1) and (2) is illustrated below. This model is known as the  $\pi$ -model for a two-winding transformer.



In the initial analysis we'll use this simplified model, assuming an almost ideal magnetic coupling ( $k \approx 1$ )

# Transformer: coupled inductors model

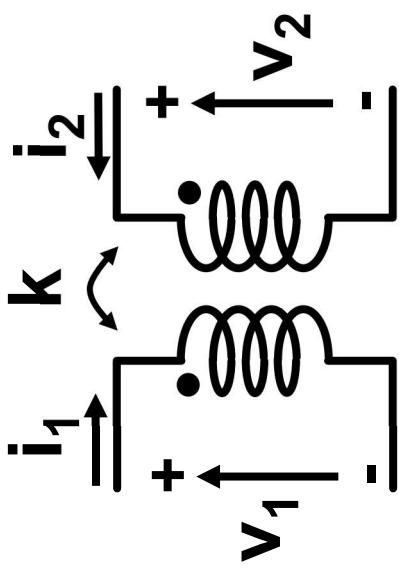

- Three parameters ( $L_1, L_2, M$ )

$$\triangleright L_1 = \frac{1}{\omega} \left( \frac{\hat{V}_1}{\hat{I}_1} \right)$$

$$\triangleright L_2 = \frac{1}{\omega} \left( \frac{\hat{V}_2}{\hat{I}_2} \right)$$

$$\triangleright M = \frac{1}{\omega} \left( \frac{\hat{V}_2}{\hat{I}_1} \right)$$


- No direct influence of  $N_1, N_2$  evident

$$\text{Note: coupling factor } k = \frac{M}{\sqrt{L_1 L_2}}$$
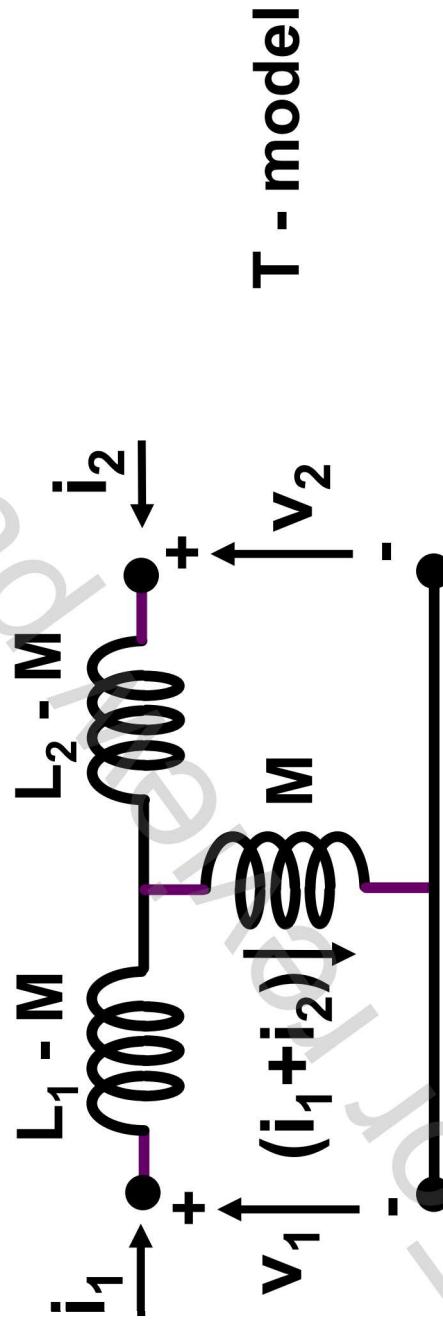
# Transformer equivalent circuit

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = (L_1 - M) \frac{di_1}{dt} + M \frac{d}{dt}(i_1 + i_2)$$


$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} = M \frac{d}{dt}(i_1 + i_2) + (L_2 - M) \frac{di_2}{dt}$$



# Introduction of a general transformation ratio n

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = (L_1 - nM) \frac{di_1}{dt} + nM \frac{d}{dt} \left( i_1 + \frac{i_2}{n} \right)$$
$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} = \frac{1}{n} \left( nM \frac{d}{dt} \left( i_1 + \frac{i_2}{n} \right) + (n^2 L_2 - nM) \frac{d}{dt} \left( \frac{i_2}{n} \right) \right)$$

Ideal transformer

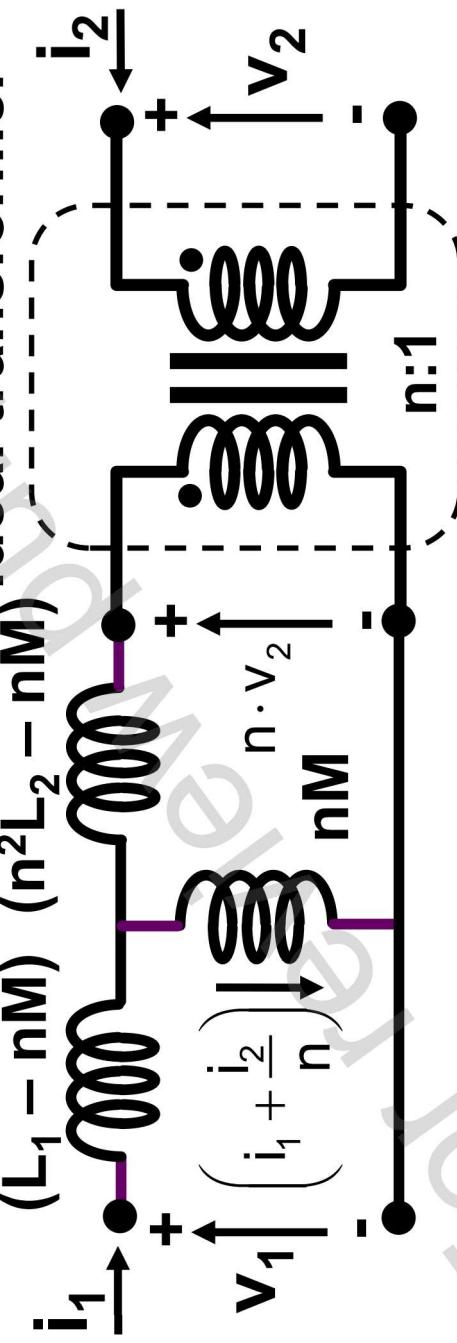


**Note:** the parameter n can be arbitrarily chosen, generating an infinite array of circuit models with the same terminal characteristics!
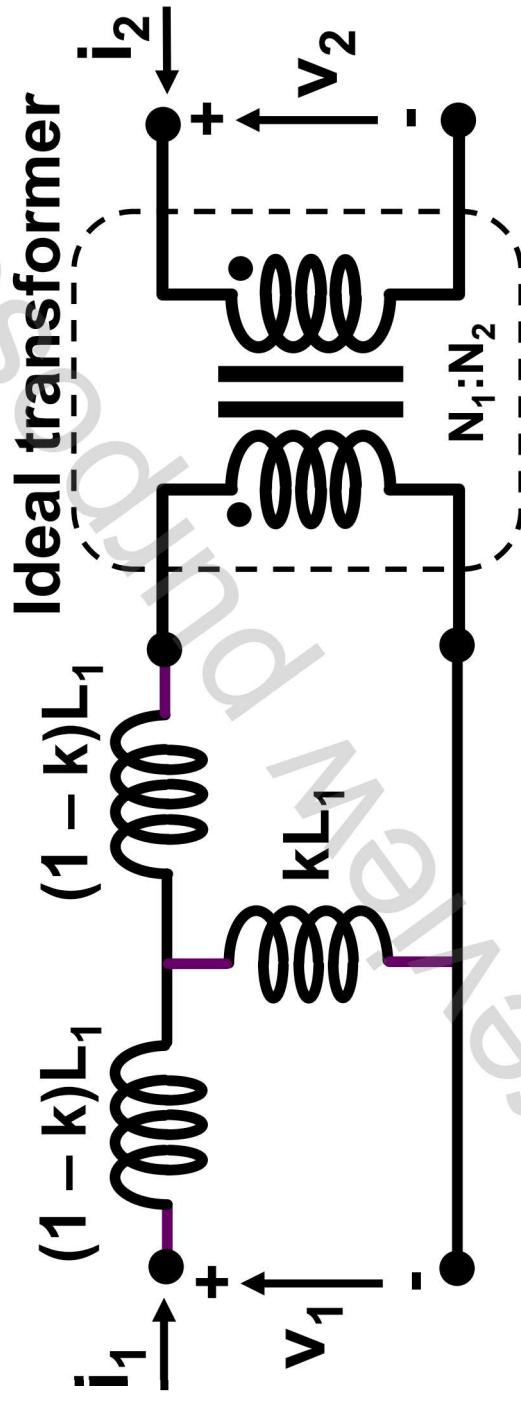
# Choice #1

$$n = \sqrt{\frac{L_1}{L_2}} \approx \frac{N_1}{N_2} \quad \text{if } k \text{ is close to 1}$$


With this choice,  $n$  is almost equal to the physical turn ratio



- Similar to the  $\pi$  - model ( $L_{12}$  transferred to the primary side)  
with  $L_m = kL_1$ ,  $L_{11} = (1-k)L_1$ ,  $L_{12} = (1-k)L_2$
- Note:  $v_2/v_1 \approx k N_2/N_1$  with secondary-side terminals open

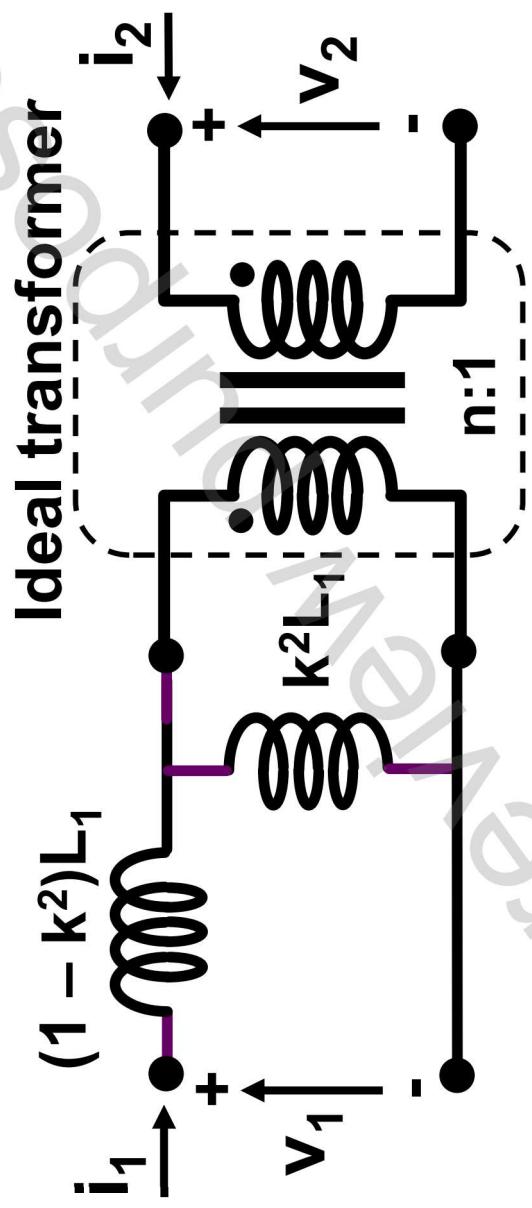
## Choice #2

$$n = k \cdot \sqrt{\frac{L_1}{L_2}} \rightarrow \text{This choice nulls the secondary leakage inductance}$$



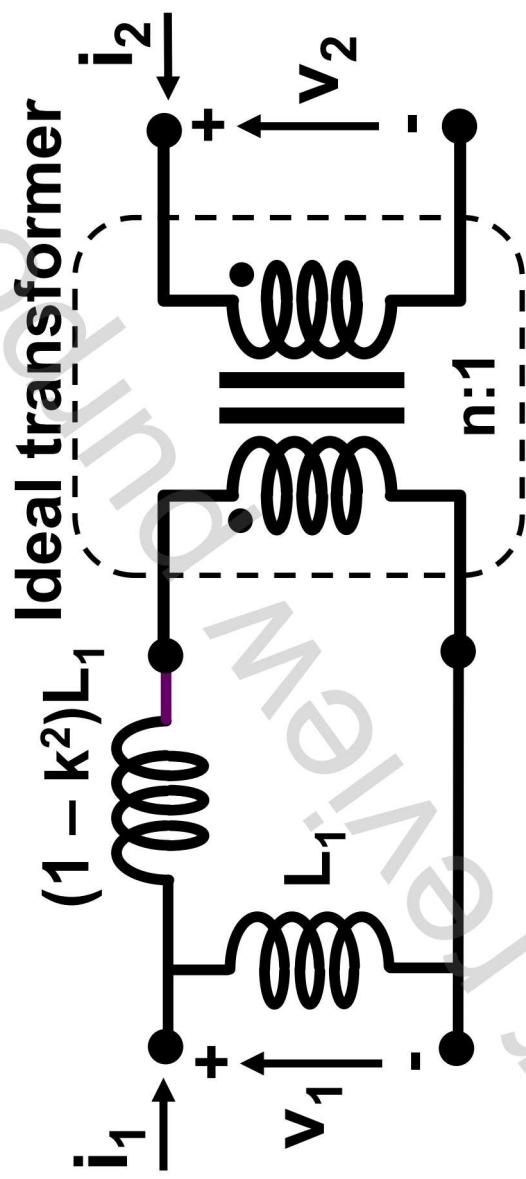
## Choice #3

$$n = \frac{1}{k} \cdot \sqrt{\frac{L_1}{L_2}} \rightarrow \text{This choice nulls the primary leakage inductance}$$



# Commonly used model ( $k$ close to 1)

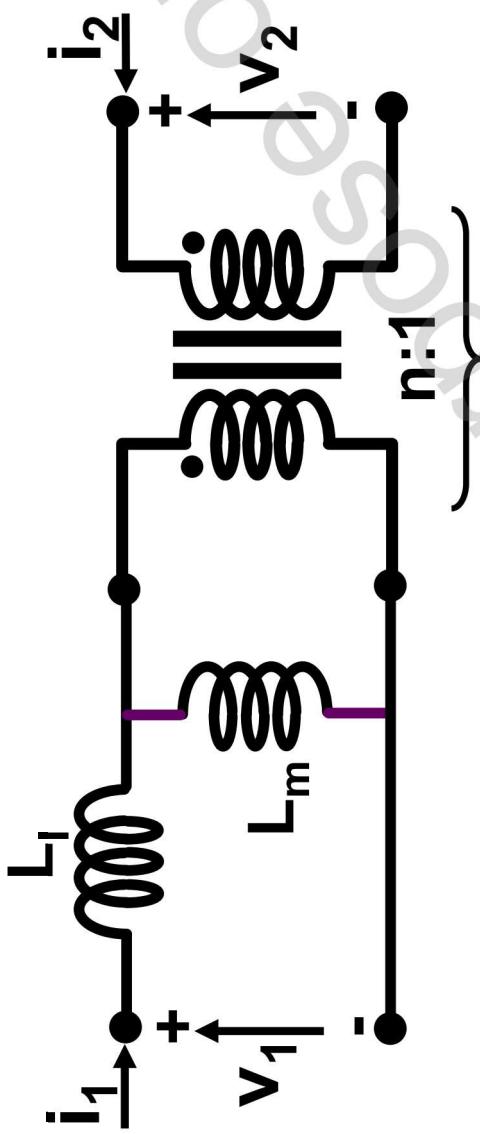


Ideal transformer

- $L_1$  is obtained by measuring the primary-side inductance with the secondary-side terminals shorted
- $L_m$  is obtained by measuring the primary-side inductance with the secondary-side terminals open.  
    ➤  $L_m = L_{\text{measured}} - L_1$

- $n$  is achieved by measuring the primary side voltage (open terminals) upon the application of a voltage to the secondary side

# Transformer core B-H characteristics


21

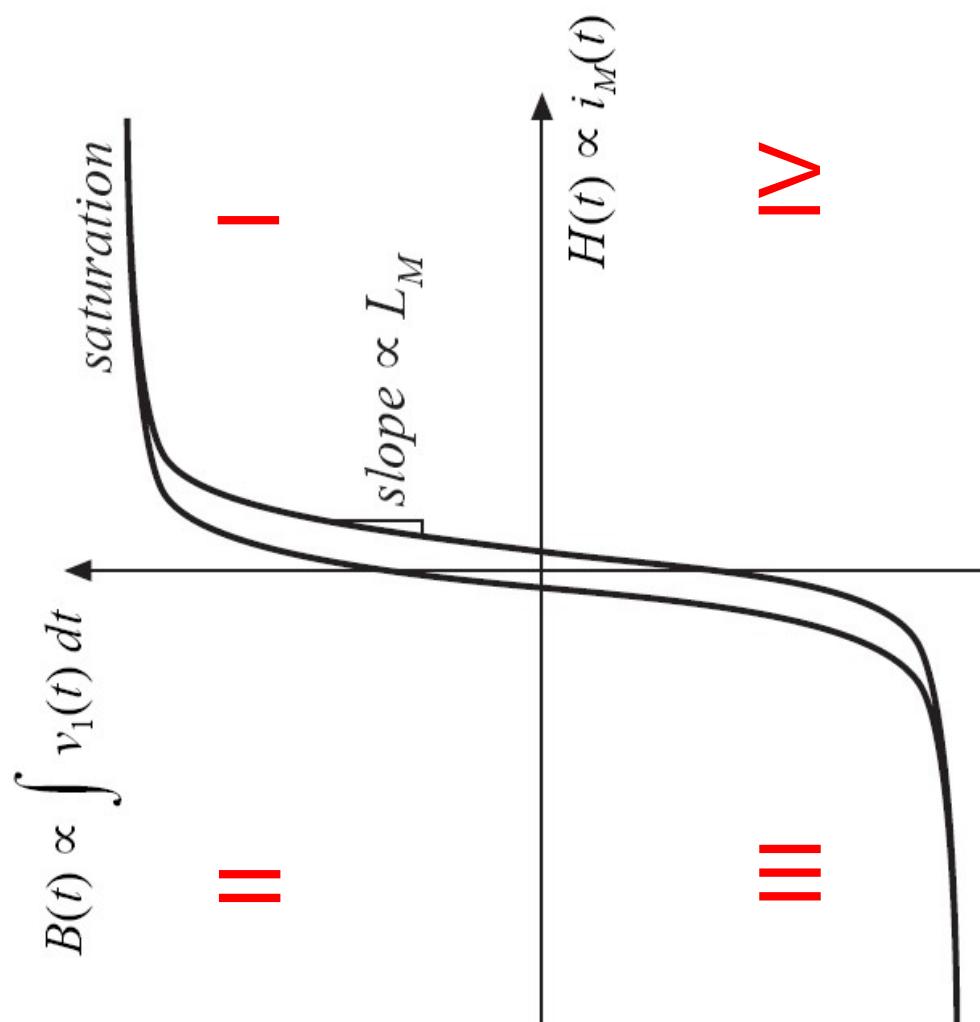

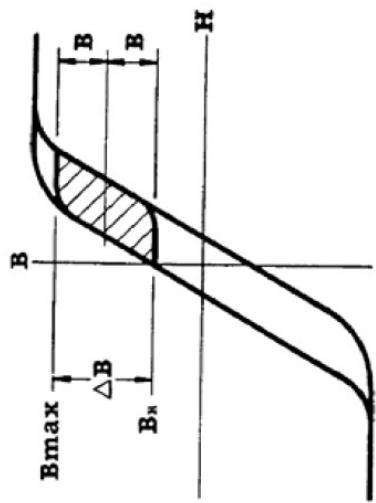
# Isolated converter topologies /1

Two kinds of core excitation for the above converters

- Unidirectional core excitation, where only the positive part (**quadrant I**) of the B-H loop is used:
  - flyback converter (derived from buck-boost converter)
  - forward converter (derived from buck converter).



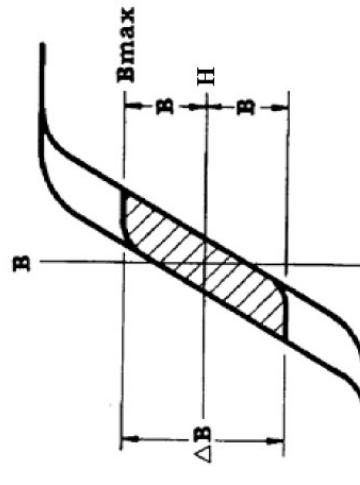
“Single-Ended”  
AC operation with DC offset



“Double-ended”  
AC-only Operation

- Bidirectional core excitation, where the positive (**quadrant I**) and the negative (**quadrant III**) parts of the B-H loop are utilized alternatively
  - push-pull converter
  - half-bridge converter
  - full-bridge converters

# Isolated converter topologies /2

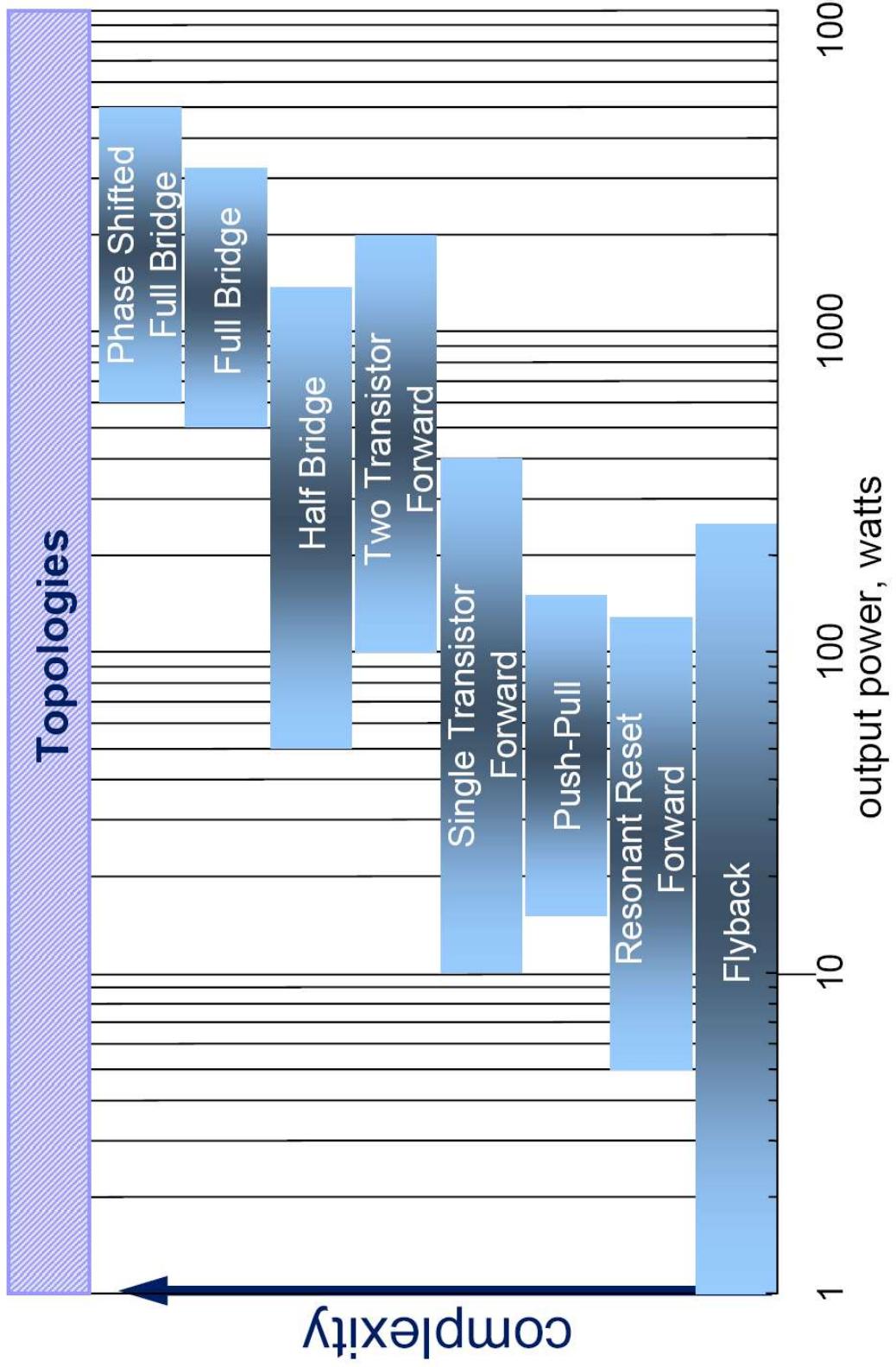

# Flyback converter

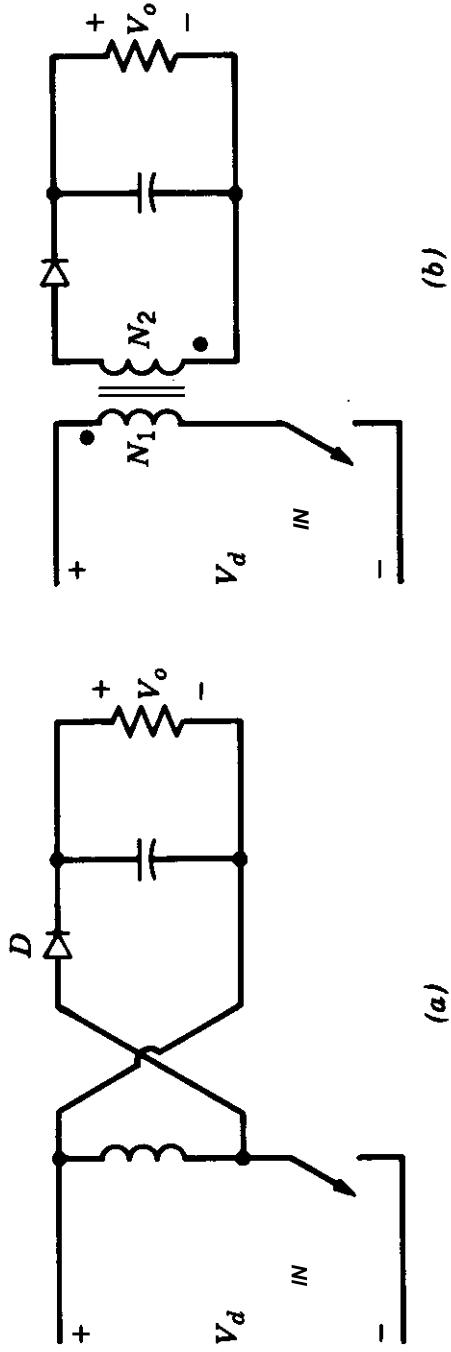


Figure 10-6 Flyback converter.

- Flyback is the most popular topology for low-power ( $< 100$  W) AC/DC conversion applications:
- a flyback transformer combines the actions of an isolating transformer and an output inductor into a single element hence, no separate inductor is needed;
- a flyback transformer provides galvanic (electrical) isolation up to  $\sim 5$  kV DC, and it can provide multiple and/or negative outputs;
- simple design requires just one semiconductor switch (MOSFET) and one freewheeling diode.

# Flyback converter: CCM

25

- During  $t_{\text{on}}$ ,  $V_{\text{in}}$  is applied to primary and current ramps up in  $L_m$ .
- As switch opens, voltage “flies back” until caught by secondary diode / cap at  $V_{\text{out}}$  on secondary side,  $= (-N_1/N_2 V_{\text{out}})$  on primary winding ( $L_m$ ).
- During  $t_{\text{off}}$ , current ramps down in  $L_m$ .



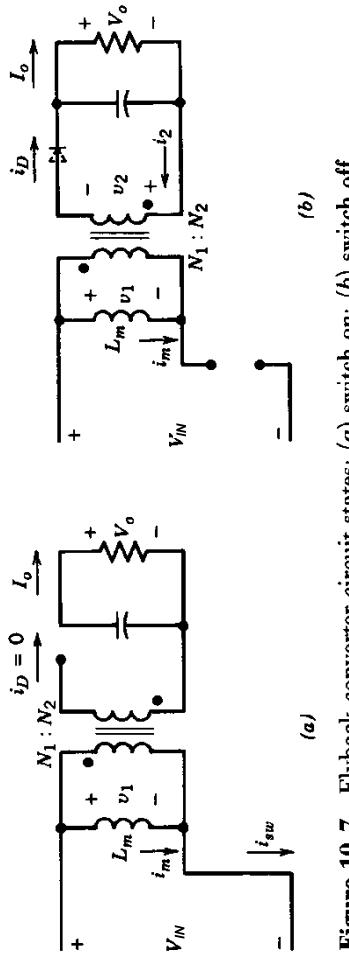
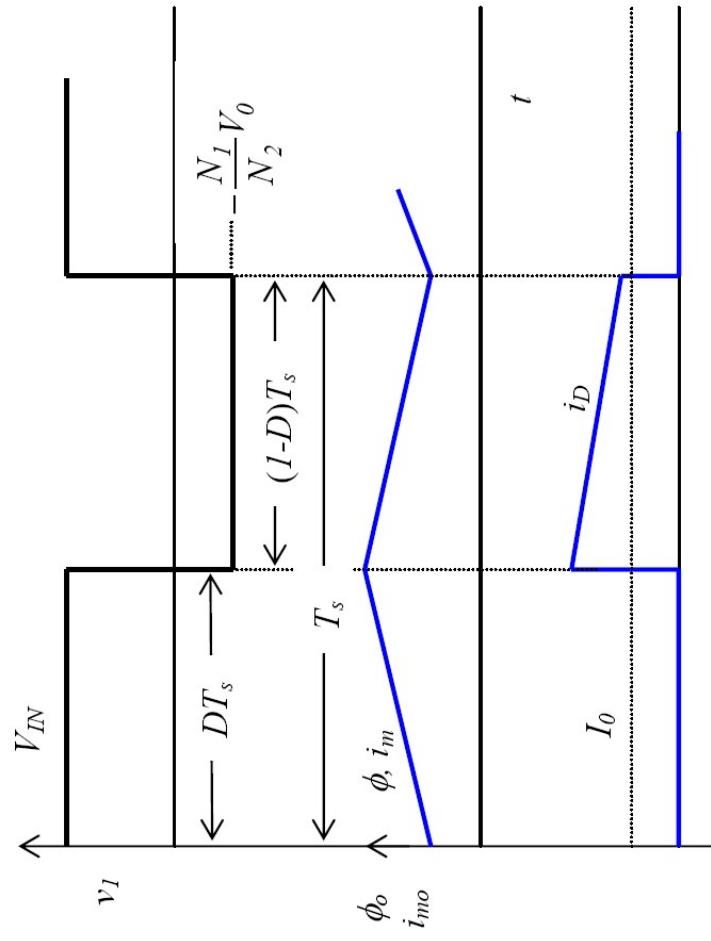


Figure 10-7 Flyback converter circuit states: (a) switch on; (b) switch off.

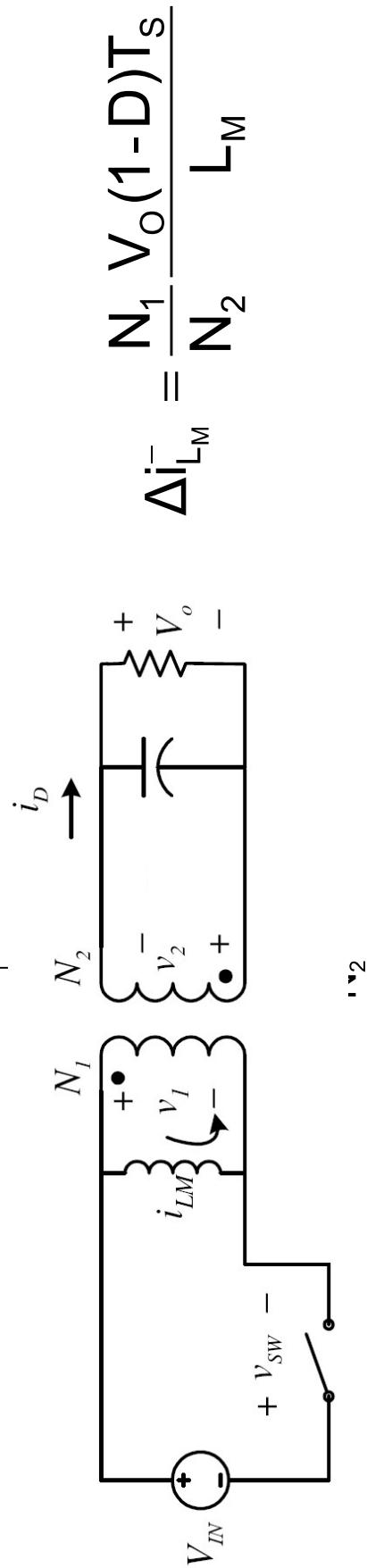

# Flyback converter: CCM

26

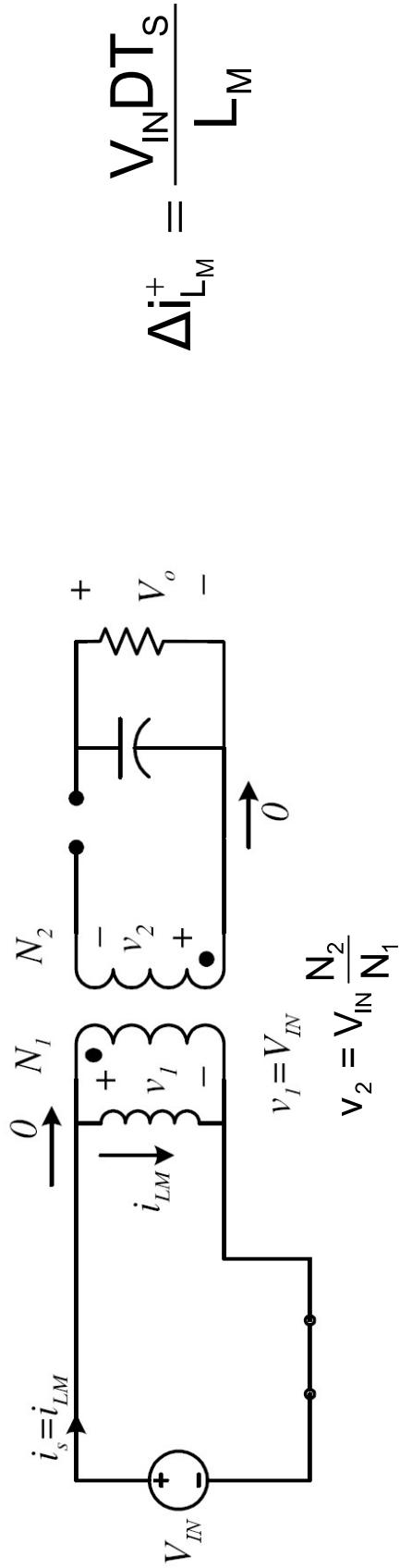

**OFF**

$$\frac{V_o}{V_{IN}} = \frac{N_2}{N_1} \frac{D}{(1-D)}$$

Input output relationship  
is similar to buck-boost  
converter.




$$\Delta i_{LM}^+ = \Delta i_{LM}^-$$

$\Delta i_{LM}^+ = \frac{V_o(1-D)}{L_M} T_S$

$\Delta i_{LM}^- = \frac{N_1}{N_2} \frac{V_o D}{L_M} T_S$

# Flyback converter: CCM waveforms

27

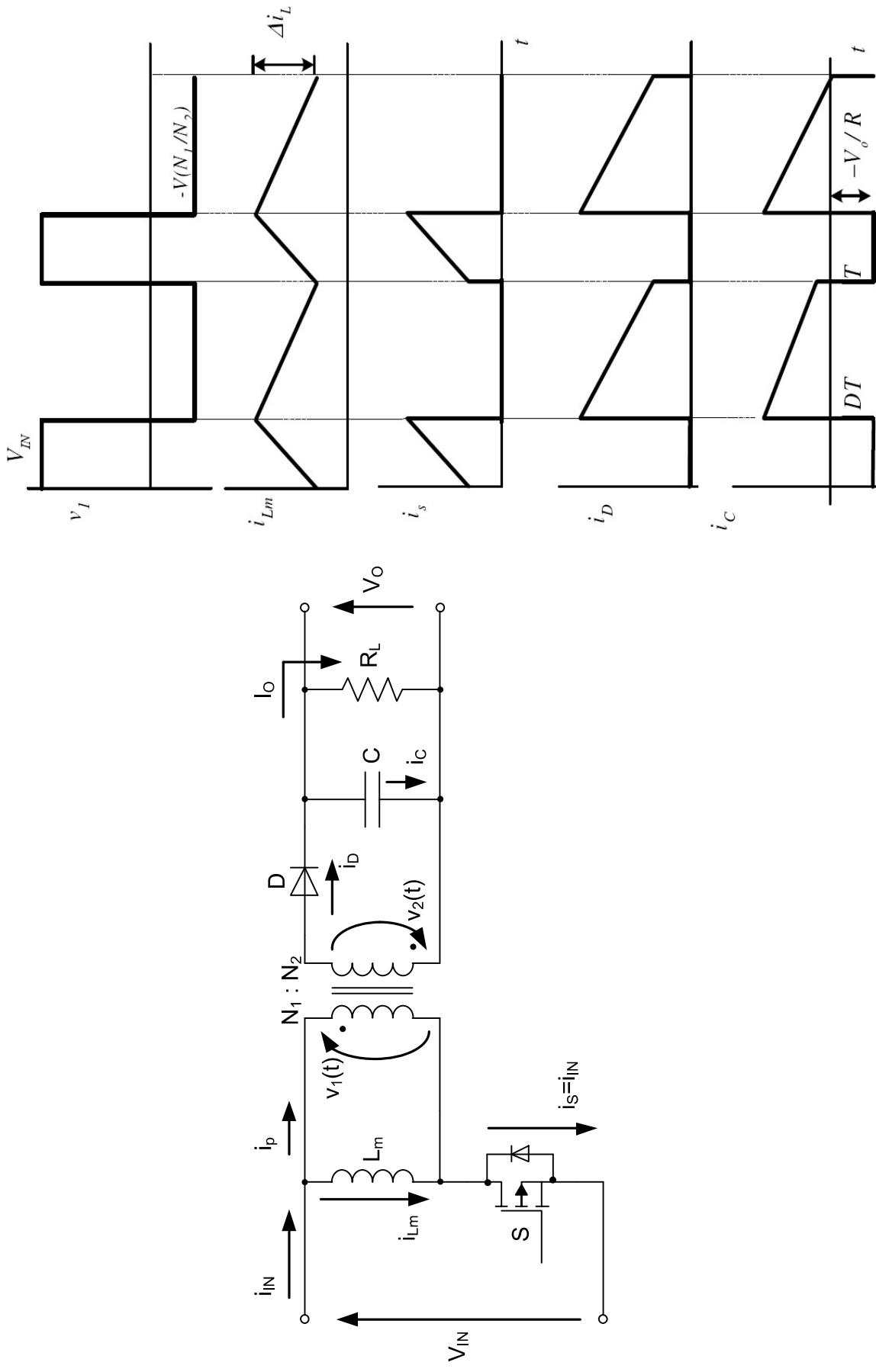

# Flyback transformer


28

- Conventional transformers store minimal energy
  - E.g. Forward converter, Push-Pull converter etc.
  - Primary and secondary currents flow simultaneously.
  - Energy is transferred by the simultaneous flow of current.
- Flyback “transformers” are really coupled-inductors
  - Primary and secondary windings do not conduct simultaneously → they can be seen as two magnetically coupled inductors → often called inductor-transformer.
  - Current flows in primary while secondary diode is reverse-biased.
  - Primary current stores energy in air-gap.
  - When primary current stops, secondary winding reverses polarity 
  - forward-biases output diode → secondary current flows.
  - Air-gap energy is transferred to the secondary load:
    - **CCM** => only some of the stored energy is delivered to the load, primary current starts before secondary current has decayed to zero;
    - **DCM** => all stored energy is delivered to the load, followed by an interval of zero current flow in both windings.

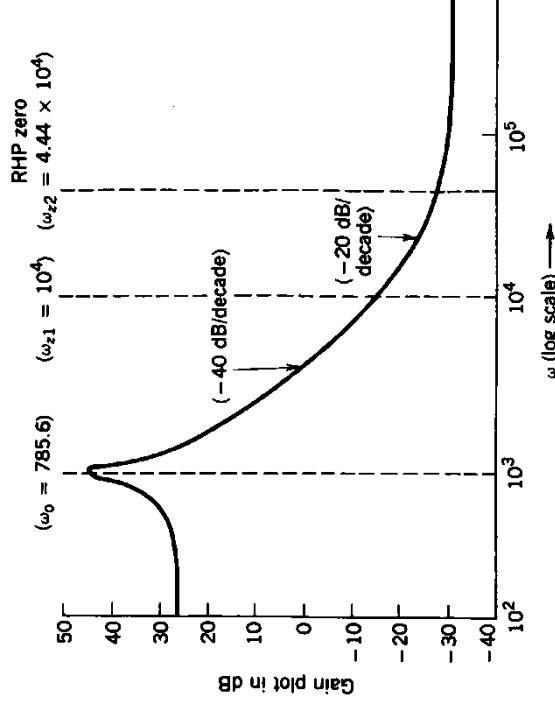
# CCM flyback converter: RHP zero

$$T_{od}(s) = \frac{\tilde{V}_o(s)}{\tilde{d}(s)} = T_{od}(0) \frac{\left(1 + \frac{s}{2\pi f_{z1}}\right) \left(1 - \frac{s}{2\pi f_{z2}}\right)}{1 + \frac{s}{2\pi f_o Q} + \left(\frac{s}{2\pi f_o}\right)^2}$$

A right half plane (RHP) zero is produced in the duty cycle-to-output transfer function when the flyback is operated in CCM.



gain

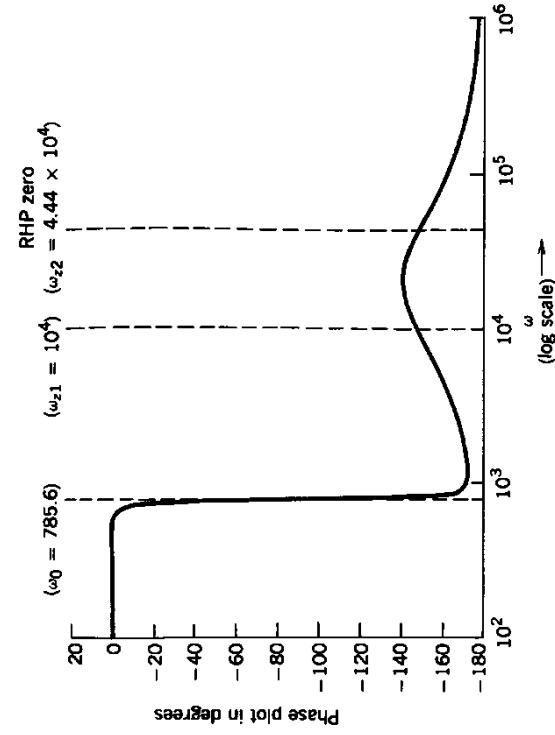

phase

# Flyback converter: CCM-DCM boundary

30

$$I_{MB} = \frac{i_{LMP}}{2} = \frac{V_{IN}DT_s}{L_m}$$

$$I_{OB} = I_D = i_{LMP} \cdot \frac{N_1}{N_2} \cdot \frac{(1-D)T_s}{2T_s} = \frac{V_{IN}D(1-D)}{2L_m f_S} \cdot \frac{N_1}{N_2}$$

Using:


$$\frac{V_o}{V_{IN}} = \frac{N_2}{N_1} \frac{D}{(1-D)}$$

we get:

$$I_{OB} = \frac{V_o \cdot (1-D)^2}{2L_m f_S} \left( \frac{N_1}{N_2} \right)^2$$

and:
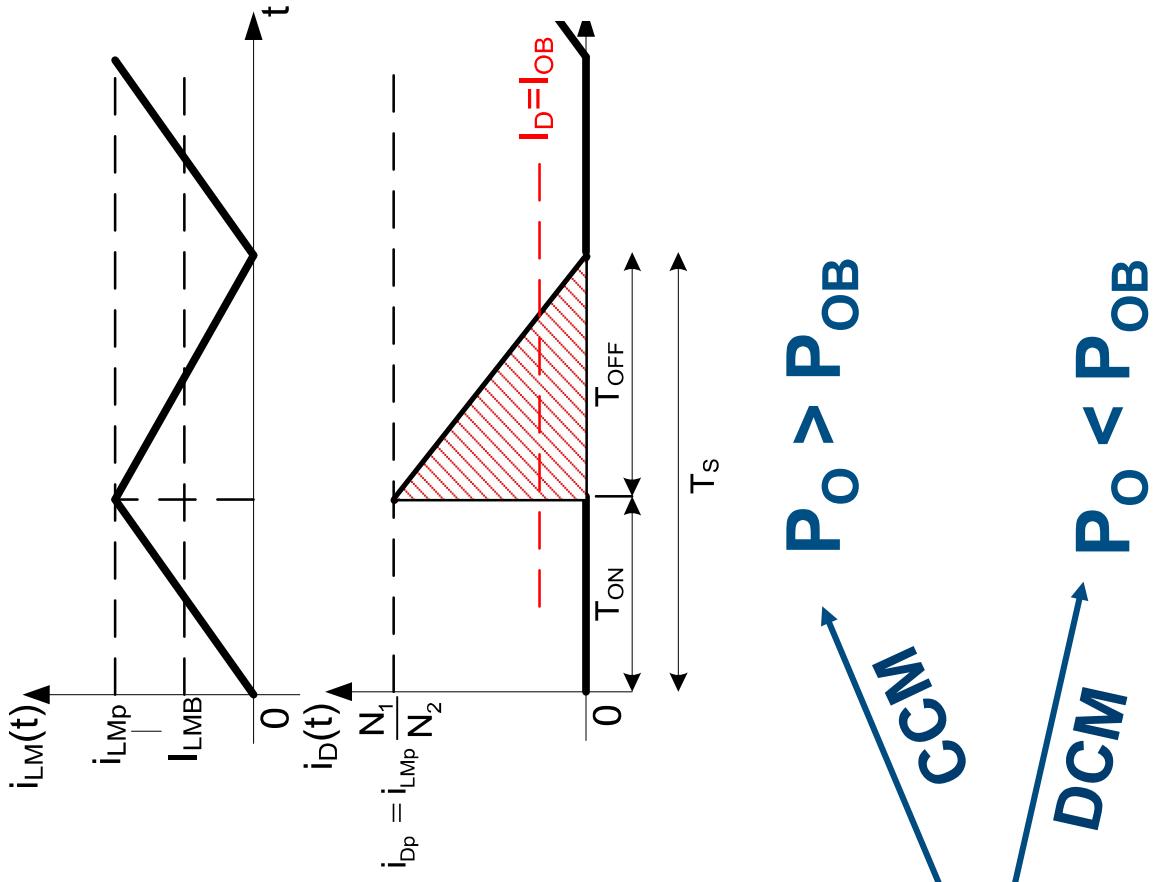
$$P_{OB} = \frac{V_o^2 \cdot (1-D)^2}{2L_m f_S} \left( \frac{N_1}{N_2} \right)^2 = \frac{V_{IN}^2 D^2}{2L_m f_S}$$



$$P_O > P_{OB}$$

CCM

$$P_O < P_{OB}$$

DCM

# Flyback converter: DCM

31

The energy transferred from the input dc voltage source  $V_{IN}$  to the magnetizing inductance during one cycle for the DCM case is:

$$W = \frac{1}{2} \cdot L_m \cdot i_{m,max}^2$$

Assuming 100% efficiency, this results in dc output power given by:

$$P_O = \frac{1}{2} \cdot L_m \cdot i_{m,max}^2 \cdot f_S = \frac{V_O^2}{R}$$



since

$$i_{m,max} = |\Delta i_m^+| = \frac{V_{IN} D}{L_m f_S}$$


it follows that

$$\frac{V_O}{V_{IN}} = D \sqrt{\frac{R}{2L_m f_S}}$$

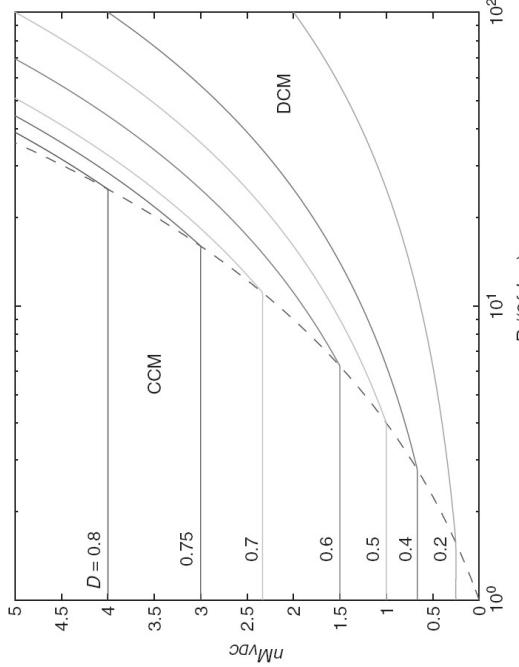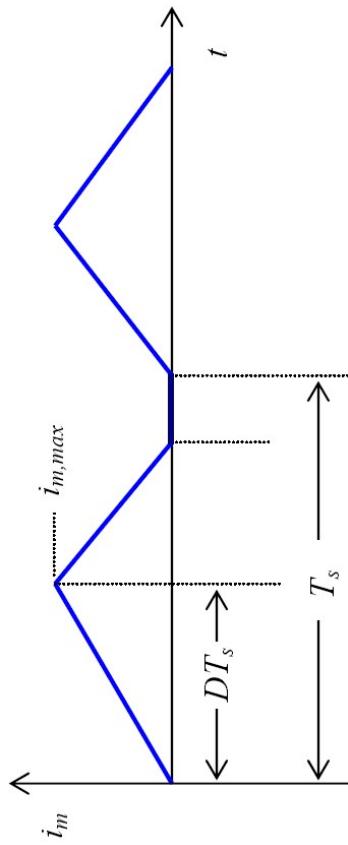Thus the feedback loop will regulate the output by decreasing D as  $V_{IN}$  or R goes up, increasing D as  $V_{IN}$  or R goes down.




# Flyback converter: DCM waveforms

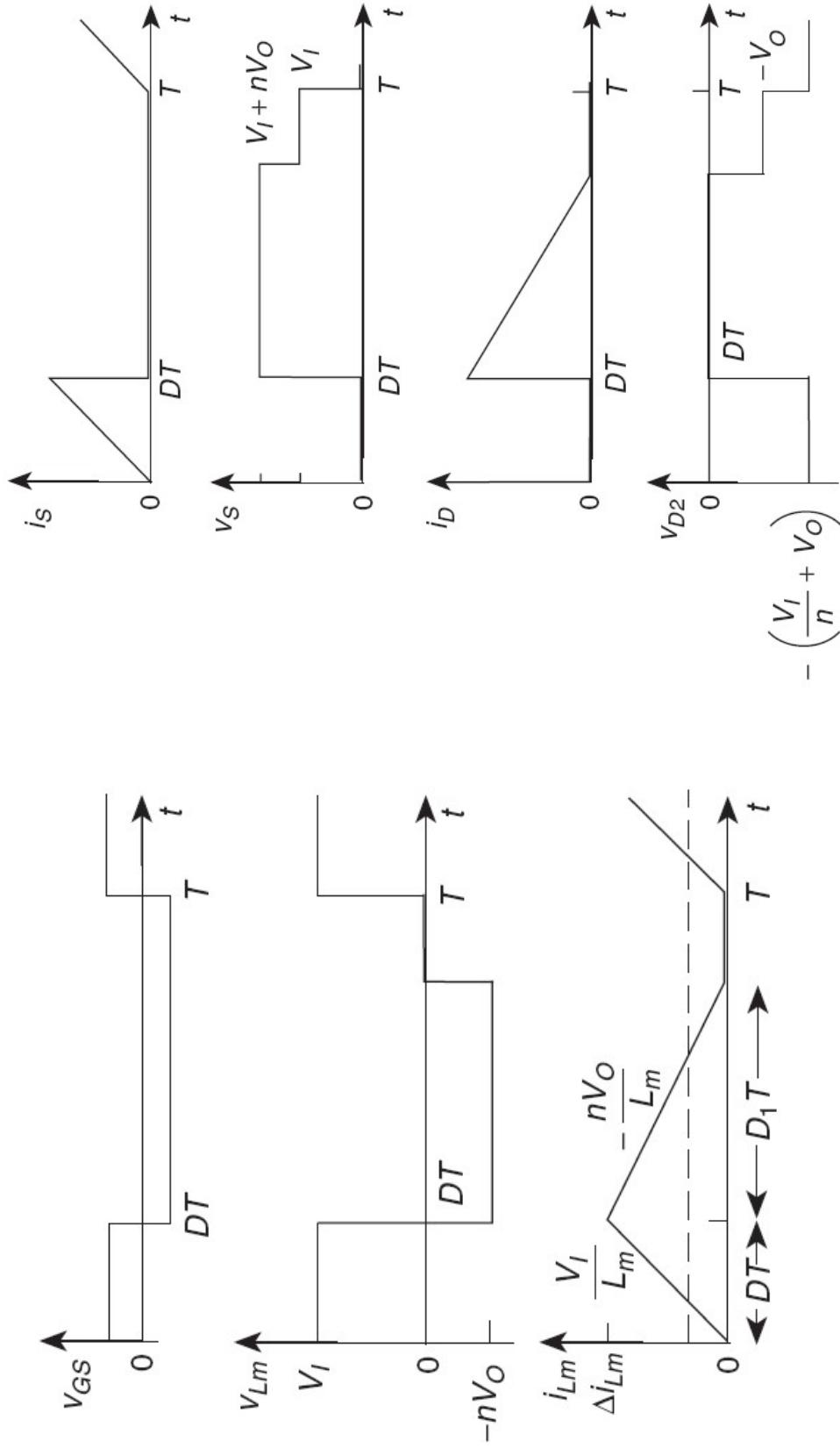

$$n = \frac{N_1}{N_2}$$

# Flyback converter: DCM vs CCM waveforms

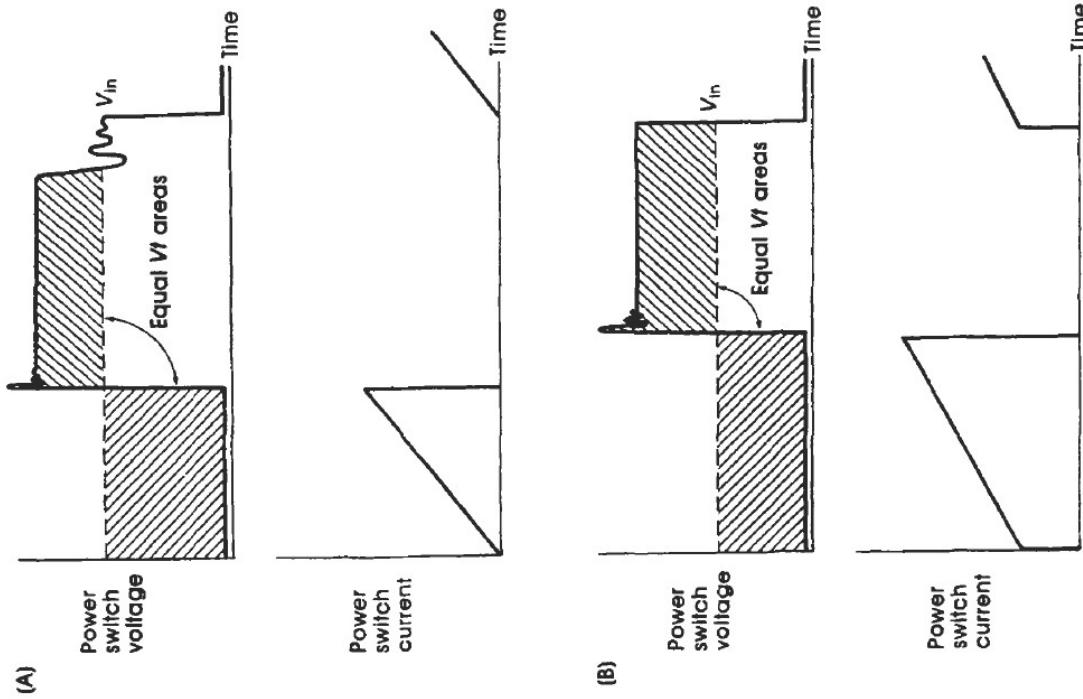

**Figure 4.6**  
(A) Flyback operating in the discontinuous mode; (B) flyback operating in the continuous mode.

# Challenges in flyback design

34

## Overall Design

- Balance cost, footprint and performance
- Design decisions on modes of operation (CCM, DCM, CRM/TM)
- Effective component selection – MOSFET, diodes should withstand the stress
- Design RC or RCD snubber to suppress ringing
- More complex design process compared to non-isolated topologies

## Transformer Design

- Customize for the specific power design specifications
- Optimize selection of transformer based on efficiency, cost, footprint
- Select appropriate core, considering loss and magnetic saturation
- Select bobbin based on physical fit
- Select wires gauge based on skin effect & current carrying capability
- Design the winding strategy

# DCM flyback converter: $L_m$ design


35

- The magnetizing inductance  $L_m$  needs to be limited to a maximum value.
- DCM ensured if:

$$P_O < P_{OB} = \frac{V_{IN}^2 D^2}{2L_m f_S} \quad \text{i.e. } L_m < \frac{V_{IN}^2 D^2}{2P_O f_S}$$

Worst conditions?  $V_{IN}$ ? D?  $P_O$ ?

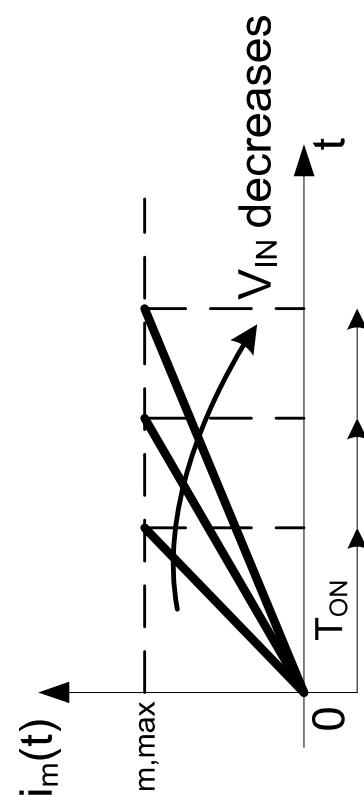
- At a given  $P_O$ ,  
 $i_{m,max} = \text{Const} = \sqrt{\frac{2P_O}{L_m f_S}}$
- The lower  $V_{IN, MIN}$ , the longer the  $T_{ON}$  needed to reach  $i_{m,max}$



# DCM flyback converter: $L_m$ design
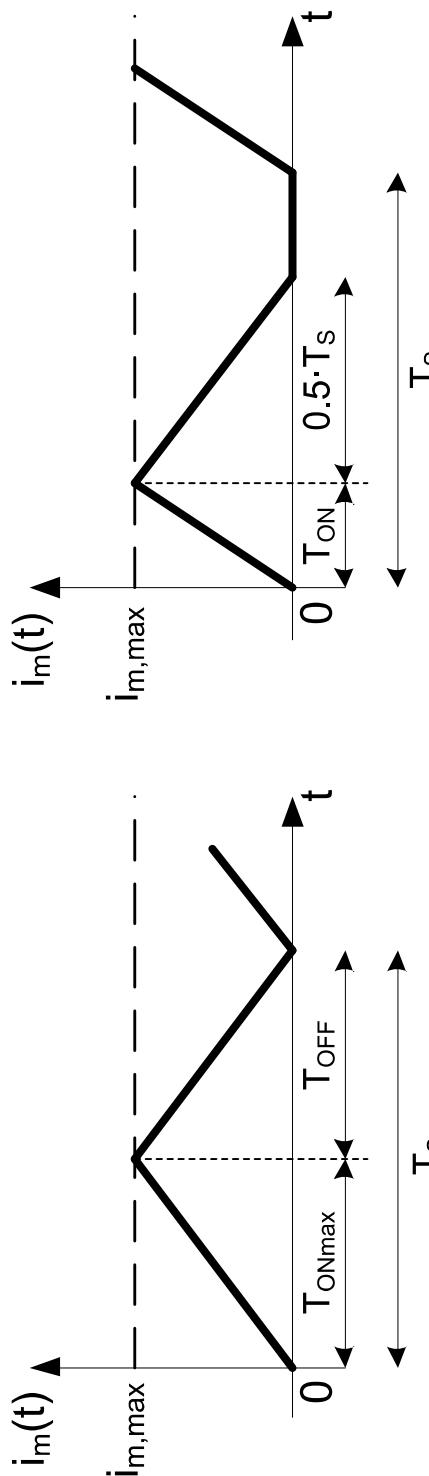
## Guidelines

- The maximum  $T_{ON}$ ,  $T_{ONmax}$  is usually set at  $0.5T_s$  (i.e.  $D_{max}=50\%$ )
- $L_m$  is designed such that  $i_m$  is able to reach  $i_{m,max}$  within  $T_{ONmax}$  in the worst conditions ( $P_{Omax}$ ,  $V_{INmin}$ )
- $N_1/N_2$  is designed such that the  $L_M$  is discharged within ( $T_s-T_{ON,max}$ )



$$V_{IN} = V_{INmin}$$

$$T_{ON} = T_{ONmax} = 0.5 T_s$$

$$V_{IN} > V_{INmin}$$

$$T_{ON} < T_{ONmax}$$

# DCM flyback converter: $L_m$ design

$$L_m \leq \frac{V_{IN\min}^2 \cdot D_{max}^2}{2 P_{Omax} \cdot f_s}$$

Assuming  
 $D_{max} = 50\%$



$$L_m \leq \frac{V_{IN\min}^2}{8 P_{Omax} \cdot f_s}$$

If converter efficiency,  $\eta$ , is taken into account, we easily get:

$$L_m \leq \frac{\eta \cdot V_{IN\min}^2}{8 P_{Omax} \cdot f_s}$$

- Assume  $\eta \sim 0.75 - 0.85$  as a first guess

# DCM flyback converter: turn ratio design

38

$$\Delta i_{L_M}^+ = \Delta i_{L_M} \quad \Rightarrow \quad \frac{V_O}{V_{IN}} = \frac{N_2}{N_1} \frac{D}{(1-D)}$$

For  $D=D_{max}=0.5$ ,  $V_{IN}=V_{INmin}$  (worst conditions) we get:

$$\frac{N_1}{N_2} = \frac{V_{INmin}}{V_O}$$

More accurately, taking into account non-idealities:

$$\frac{N_1}{N_2} = \left( \frac{V_{INmin} - V_{DSon}}{V_O + V_D} \right)$$

# Flyback regulator: design example

- Input voltage:  $V_{IN} = 36 \div 72 \text{ V}$
- Output voltage:  $V_O = 5 \text{ V}$
- DCM operation
- Output voltage ripple:  $\Delta V_O = 100 \text{ mV}$
- Output current:  $I_O = 8 \text{ A} \rightarrow P_O = 40 \text{ W}$
- Switching frequency:  $f_S = 100 \text{ kHz}$
- Closed loop bandwidth:  $f_C = 20 \text{ kHz}$

# Flyback regulator: design example

40

**Step 1:** determine the turn ratio

$$\frac{N_1}{N_2} = \left( \frac{V_{IN\min} - V_{DSon}}{V_O + V_D} \right) \approx 6 \quad \text{Assume } V_d \text{ and } V_{DSon} \sim 1V$$

**Step 2:** determine switch voltage rating

$$BV_{DSmin} > V_{INmax} + \frac{N_1}{N_2} \cdot V_O = 102 \text{ V}$$

Power MOS

$$BV_D > \frac{N_2}{N_1} \cdot V_{INmax} + V_O = 17 \text{ V}$$

diode

# Flyback regulator: design example

**Step 3:** determine the magnetizing inductance

$$L_m \leq \frac{\eta \cdot (V_{IN\min} - 1)^2}{8 P_O \cdot f_s} \approx 30 \mu H \quad (\text{assume } \eta=0.8)$$

**Step 4:** determine the peak primary current in order to fully specify the power switch

$$i_{p,\max} = i_{m,\max} = \frac{(V_{IN\min} - 1) \cdot D_{\max}}{L_m f_s} = 5.72 A$$

Select a power MOS with a  $r_{DSon}$  such that:

$$r_{DSon} \cdot i_{m,\max} \leq 1V \rightarrow r_{DSon} \leq 175 m\Omega$$

# Flyback regulator: design example

**Step 5:** determine the size of the core

$$L_m i_{p,\max}^2 = 1 \text{ mH A}^2$$

A Kool Mu™ distributed-gap core is suitable for our design.  
Going up the selector chart from 1 mH A<sup>2</sup> yields a 77210 core  
with 90μ (aggressive design). A<sub>L</sub> = 49nH/T<sup>2</sup>±8%.

**Step 6:** calculate primary turns N<sub>1</sub>

$$N_1 = \sqrt{1000 \frac{L_m (\mu H)}{(A_L \cdot 1.08)}} = 23.8 \text{ T} \quad (\text{use } 23 \text{ T})$$

# Flyback regulator: design example

43

**Step 7:** calculate magnetizing force to make sure core does not saturate

From the 77210 data sheet we see that  $A'_L = 36.5 \text{ AT}$  with 23 Turns. Adjust turns accordingly:

$$N'_1 = N \frac{A'_L}{A_L} = 30.4 \text{ T} \quad (\text{use } 30 \text{ T})$$

Using 30 Turns would give  $L_m \sim 30 \mu\text{H}$  in the worst condition.

**Step 8:** calculate secondary turns  $N_2$


$$N_2 = \frac{N'_1}{6} = 5 \text{ T}$$

# Flyback regulator: design example

44
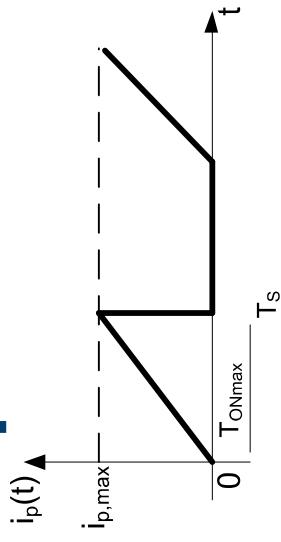
## Step 9: primary wire size

$$I_{P(\text{rms})} = \frac{I_{p,\text{max}}}{\sqrt{6}} = 2.34 \text{ A}_{\text{rms}}$$



From the wire table we see that #20 AWG is appropriate, but..

### ➤ Skin effect

to minimize skin effect the selected wire diameter should not exceed  $2 \cdot \delta$ , where  $\delta$  is the skin depth of copper.

### ➤ Winding Considerations


- Tight coupling between the primary and secondary windings is mandatory to minimize Lleak.
- It is best to wind the core by using a "multi-filar" type of winding. The bundle of wires (having the same length) can be wound on the core at one time by laying the wires "side-by-side" ..
- As a general rule, the more strands and the smaller the wire gauge, the less the leakage inductance and the tighter the coupling between windings.

Hence, use 3 strands - #25 AWG    30 Turns for primary winding.
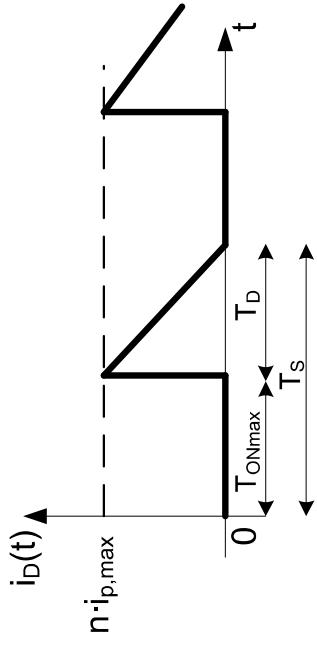
# Flyback regulator: design example

**Step 10:** secondary wire size

$$I_{S(\text{rms})} = \frac{N_1}{N_2} \frac{i_{p,\text{max}}}{\sqrt{6}} \approx 14 \text{ A}_{\text{rms}}$$



Use 7 strands - #21 AWG    5 Turns for secondary winding.

**Step 11:** building of core

Check the winding factor, WF

$$WF = \frac{(N_1 \cdot n_{w1} \cdot A_{w1} + N_2 \cdot n_{w2} \cdot A_{w2})}{\text{Window Area}} = \frac{(30 \cdot 3 \cdot 2 \times 10^{-3} \text{ cm}^2 + 5 \cdot 7 \cdot 4.84 \times 10^{-3} \text{ cm}^2)}{1.14 \text{ cm}^2} \cong 30\%$$


Conclusion for core design

Use 77210 core with 30T of 3 - #25AWG in parallel for the primary and 5T of 7 - #21AWG in parallel for the secondary.

# Flyback regulator: design example
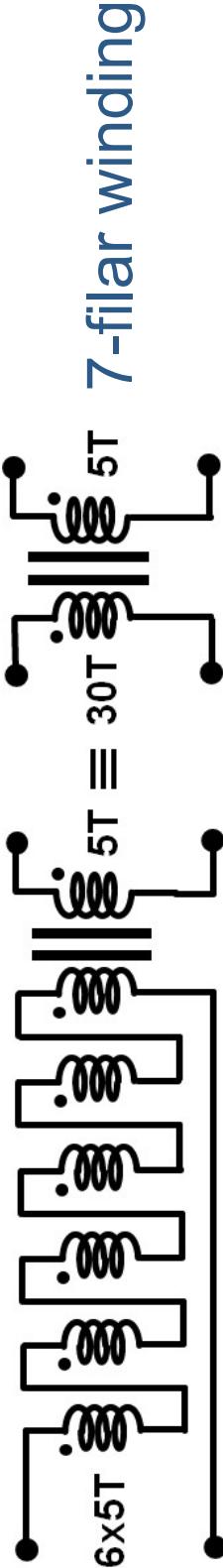
## Step 12: windings

- We have 30T on the primary and 5T on the secondary.
- We can break the primary up into a series of sections (see figure) so that we can wind both the primary and secondary in a “*multi-filar*” fashion (single bundle).
- Since  $5 \times 6 = 30$ , we need 6 series connection for the primary.
- Hence, we take  $6 \times 3 = 18 - \#21\text{AWG}$  with 7 - #21AWG, combine them in a bundle and wind 5T around the core. Then connect the primary in series to make the 30 Turns.




**5T, 6 sections in series = 30T equivalent**

- The advantages are twofold: all wires are of equal length and the interwinding coupling is improved.
- The disadvantage is that the turns ratio must always be an integer number.
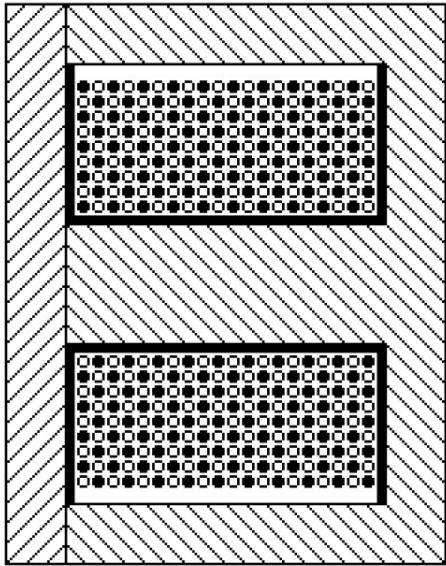
# Winding Techniques:recap


47

- The best coupling is achieved with a one-to-one layout, meaning that the primary and secondary are wound together as a twisted-pair wire in one layer on a bobbin (**multi-filar winding**). This is possible, however, when the turns ratio is an integer number.



● = PRIMARY   ○ = SECONDARY

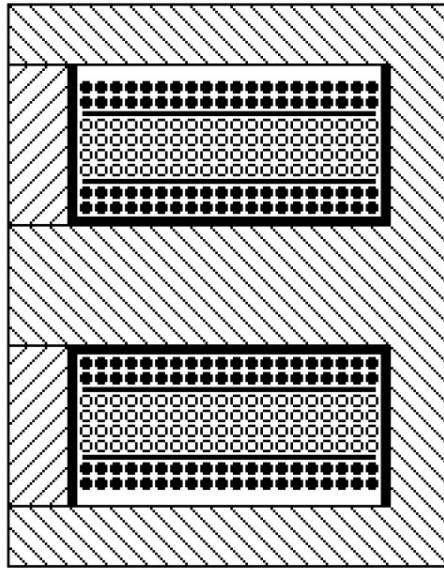- When a fractional ratio is required, a "standard" winding technique is used, where the windings are placed separately on the core. Interleaving the winding is a good way to go.



● = PRIMARY   ○ = SECONDARY


*Note: for a deeper insight on transformer design see  
Erickson, ch. 13 and Mohan, ch. 30*

# Flyback regulator: design example

48

## Step 13: output capacitor

Neglecting the capacitive ripple:

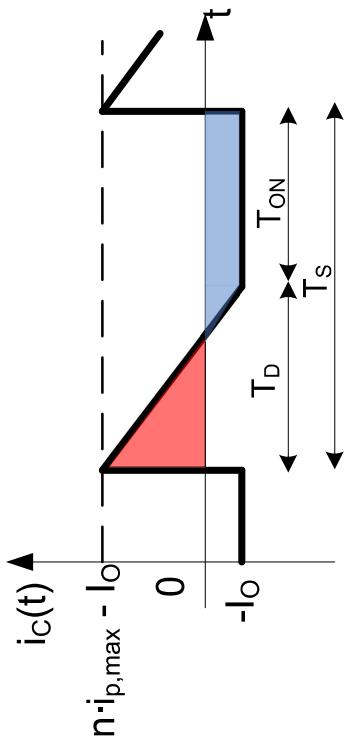

$$\Delta V_O = ESR \cdot \Delta i_C = ESR \cdot \frac{N_1}{N_2} \cdot i_{p,\max} \leq 100mV \quad \rightarrow \quad ESR < 2.9m\Omega$$

For instance, use 10 Sanyo "10SVP330M" OS-CON capacitors in parallel ( $C=330\mu F$ ,  $ESR=17m\Omega$ , rated ripple current=3.95 A<sub>rms</sub>).


$$C_{TOT} = 3300\mu F, ESR_{TOT} = 1.7m\Omega$$

$$\Delta V_O = \Delta V_C + \Delta V_{ESR} \approx 74mV$$
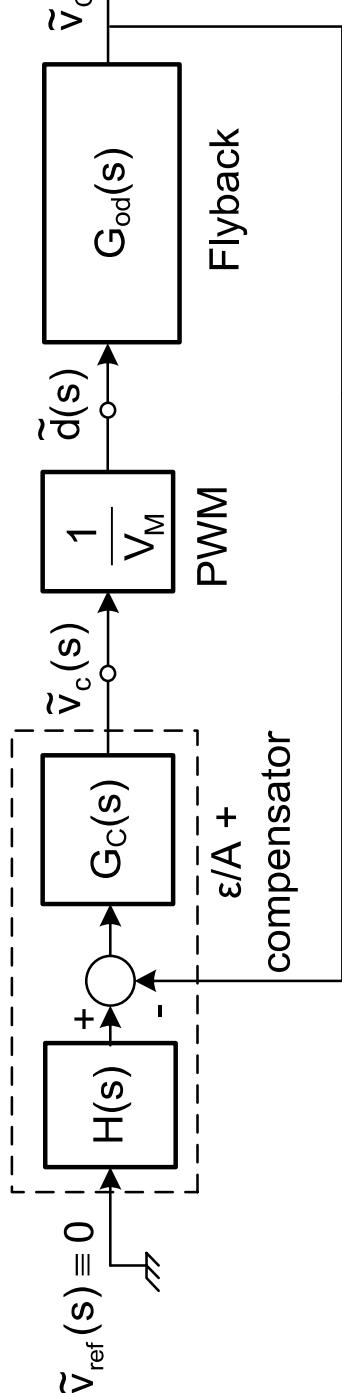
# Flyback regulator: design example

49

Step 14: closing the feedback loop (voltage mode control)



In DCM:


$$G_{\text{od}}(s) = \frac{\tilde{V}_O(s)}{\tilde{d}(s)} = G_{\text{od}}(0) \frac{1 + \frac{s}{2\pi f_z}}{1 + \frac{s}{2\pi f_p}}$$

$$f_p = \frac{2}{2\pi \cdot R \cdot C} = \frac{1}{\pi \cdot R \cdot C}$$

# Flyback regulator: design example
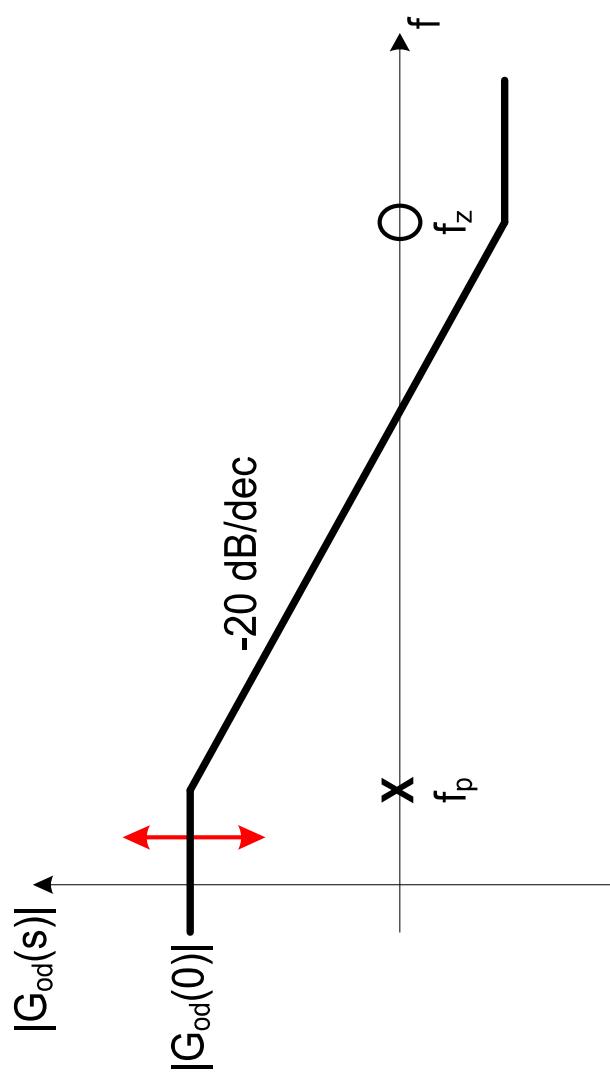
## Note

- $G_{od}(0)$  depends on  $V_{IN}$
- the pole frequency,  $f_p$ , is fixed:
  - with  $I_O = 8 A$  we have  $R = 0.625 \Omega$ , giving  $f_p \approx 154 \text{ Hz}$



# Flyback regulator: design example

Control-to-output transfer function

$$G_{OC}(s) = \frac{\tilde{V}_o(s)}{\tilde{V}_c(s)} = G_{od}(s) \cdot G_M(s) = \frac{G_{od}(0)}{V_M} \frac{1 + \frac{s}{2\pi f_z}}{1 + \frac{s}{2\pi f_p}}$$


For instance,  $V_M=2.5$  V for a UC1524A controller. Therefore:

$$G_{OC}(0) = \frac{\tilde{V}_o(0)}{\tilde{V}_c(0)} = \frac{V_{IN}}{V_M} \sqrt{\frac{R}{2L_m \cdot f_s}} \approx 0.129V_{IN}$$

►  $G_{OC}(0)|_{max} = 9.29$  for  $V_{IN}=V_{INmax}$

►  $G_{OC}(0)|_{min} = 4.64$  for  $V_{IN}=V_{INmin}$

# Flyback regulator: design example

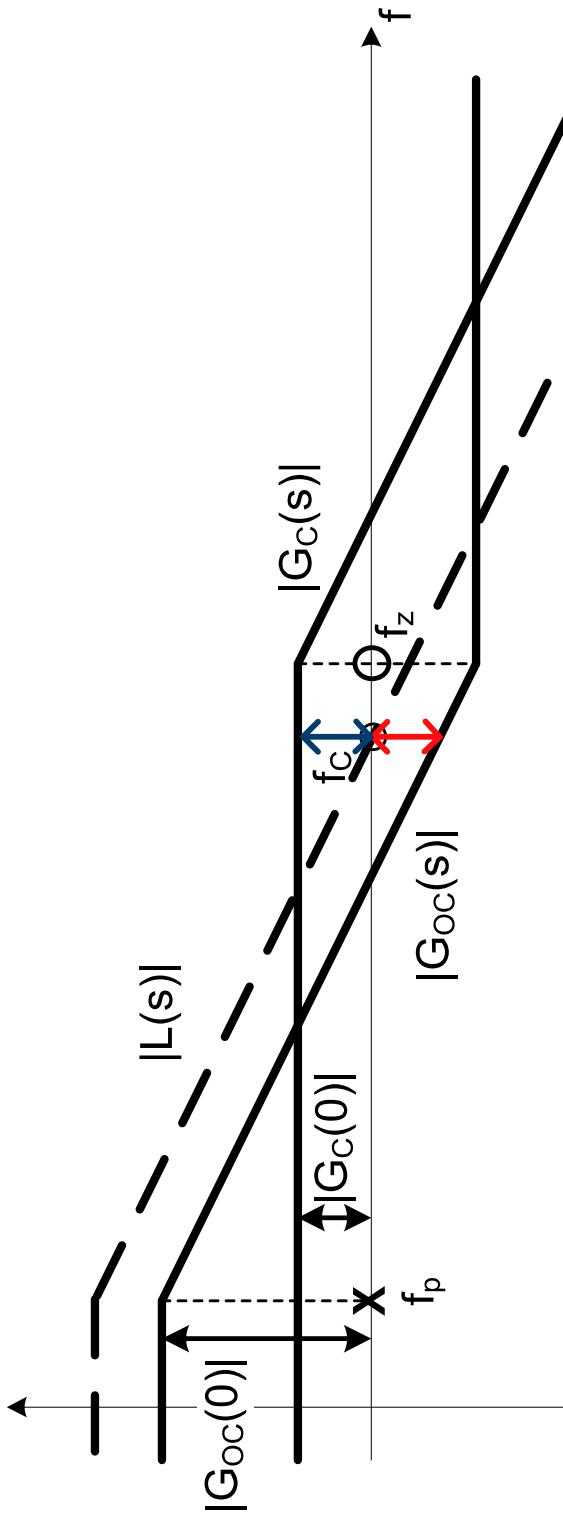


Simple first-order low pass compensation network

- compensation pole used to cancel ESR zero
- set the crossover frequency (0 dB loop gain) at the desired value ( $f_c = f_s/5 = 20$  kHz) by adjusting  $G_c(0)$

# Flyback regulator: design example

53

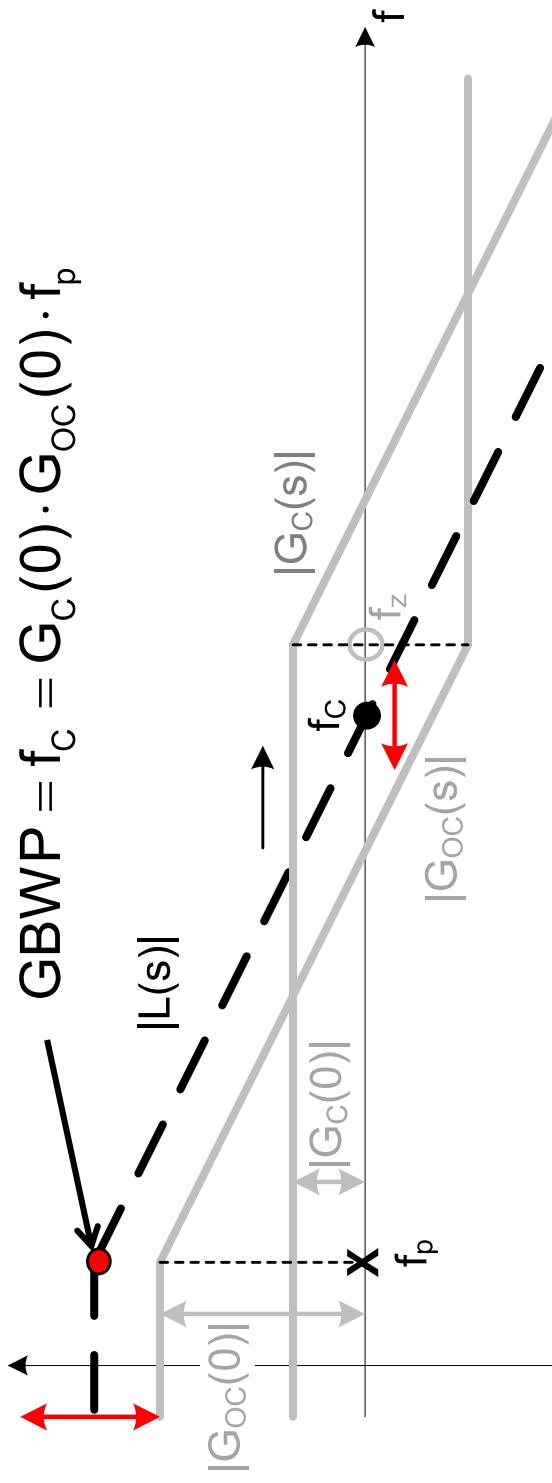

► Worst condition for  $G_{OC}(0) = G_{OC}(0)|_{max} = 9.29$

► Using GBWP



$$f_{C_{MAX}} = G_C(0) \cdot G_{OC}(0)|_{max} \leq \frac{f_{SW}}{5} = 20\text{kHz}$$

$$\left. \begin{array}{l} G_C(0) \leq 13.96 = 23\text{dB} \\ G_{OC}(0)|_{max} = 9.3 = 19.35\text{dB} \\ |L(0)|_{max} = 42.35\text{dB} \end{array} \right\}$$

# Flyback regulator: design example

54

- Compensation network

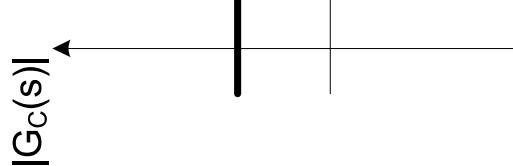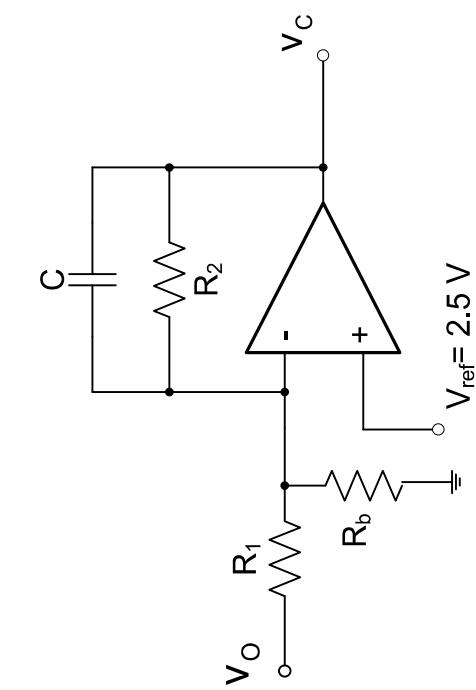


$$G_C(0) = \frac{R_2}{R_1} \quad f_{z\text{ESR}} = \frac{1}{2\pi R_2 C}$$

- Use for instance:

- $R_1 = 2.8 \text{ k}\Omega$
- $R_b = 2.8 \text{ k}\Omega$
- $R_2 = 39 \text{ k}\Omega$
- $C = 150 \text{ pF}$

May want to consider a second capacitor in series with  $R_2$

# $L(s)$ : Bode diagram

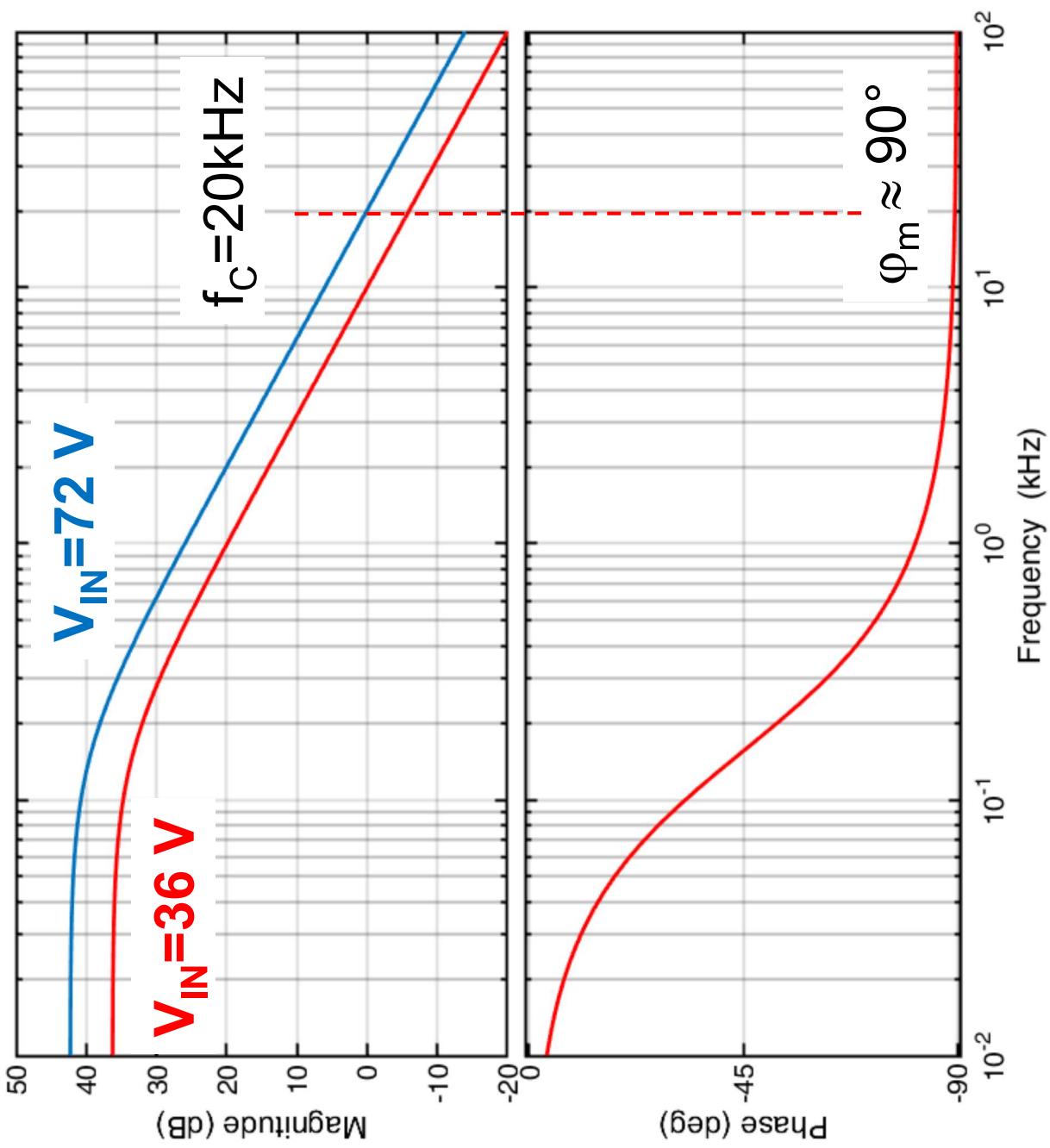

# Flyback regulator: design example

56

- Efficiency check

$$\eta = \frac{P_o}{P_o + \sum P_{\text{loss}}} \quad \text{with } P_D = I_{O,n\max} \cdot V_D \approx 8 \text{ W}, \quad P_{\text{TRANSF}} \approx 1.7 \text{ W}, \quad P_{\text{sw}} = 0.9 \text{ W}$$

$$\text{resulting in } \eta = \frac{P_o}{P_{\text{IN}}} = 0.79 ! \quad \text{No need for a 2<sup>nd</sup> iteration.}$$

Note: power dissipation mainly comes from the diode. Solutions?

- Minimum duty-cycle check


$$\boxed{D_{\min} = \frac{V_o}{V_{\text{IN}}} \sqrt{\frac{\eta \cdot R}{2L_m f_s}} \approx 24\%}$$

# Flyback regulator: leakage inductance

57

- Leakage inductance overvoltage


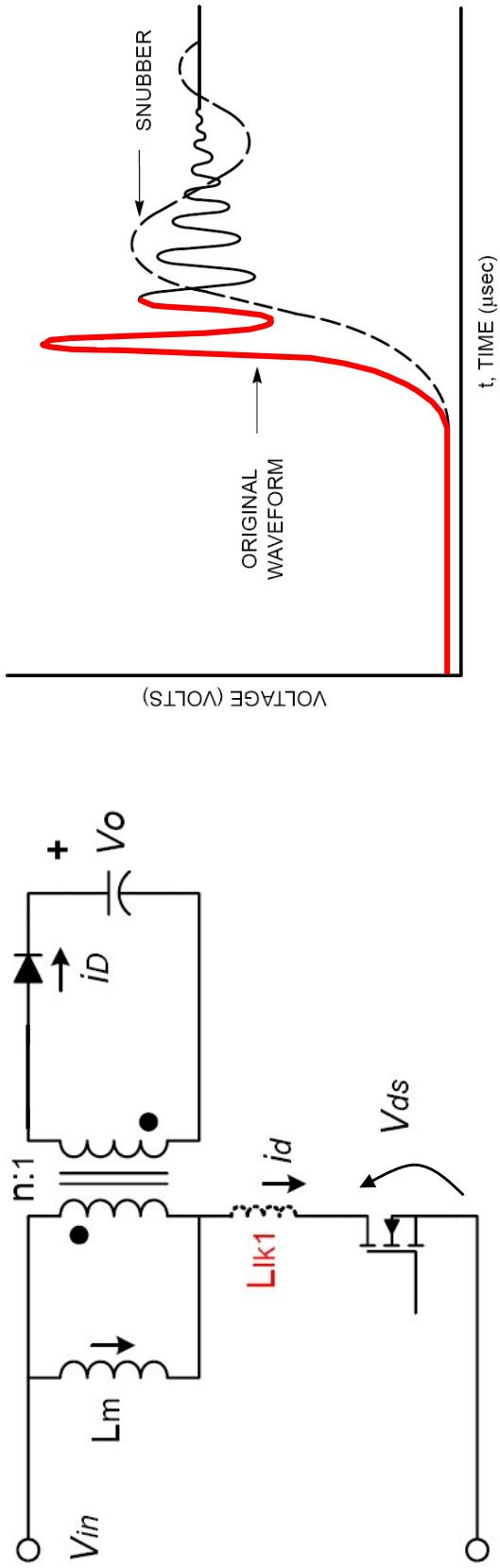
When the power MOSFET is turned off, there is a high voltage spike on the drain due to the transformer leakage inductance. This excessive voltage on the MOSFET may lead to an avalanche breakdown and eventually failure of power MOSFET. Therefore, it is necessary to use an additional network to clamp the voltage.



# Flyback regulator: leakage inductance

58


- Clamp networks

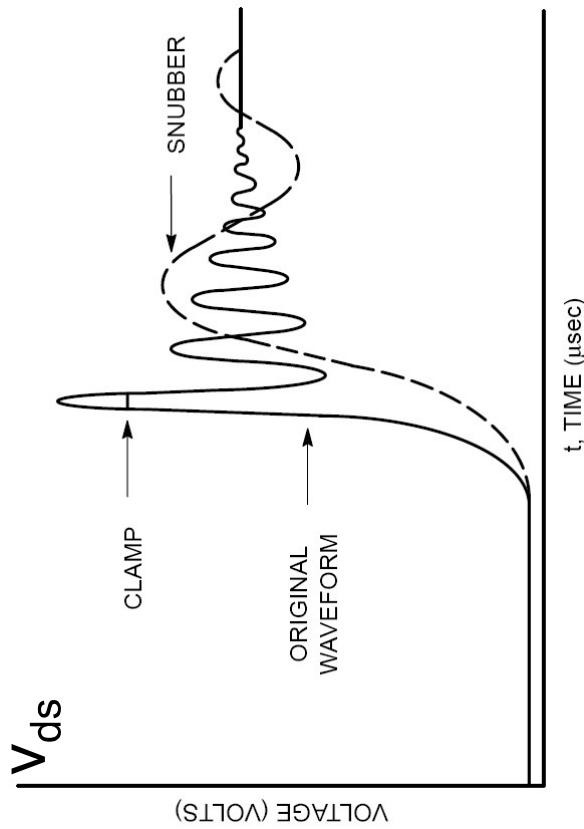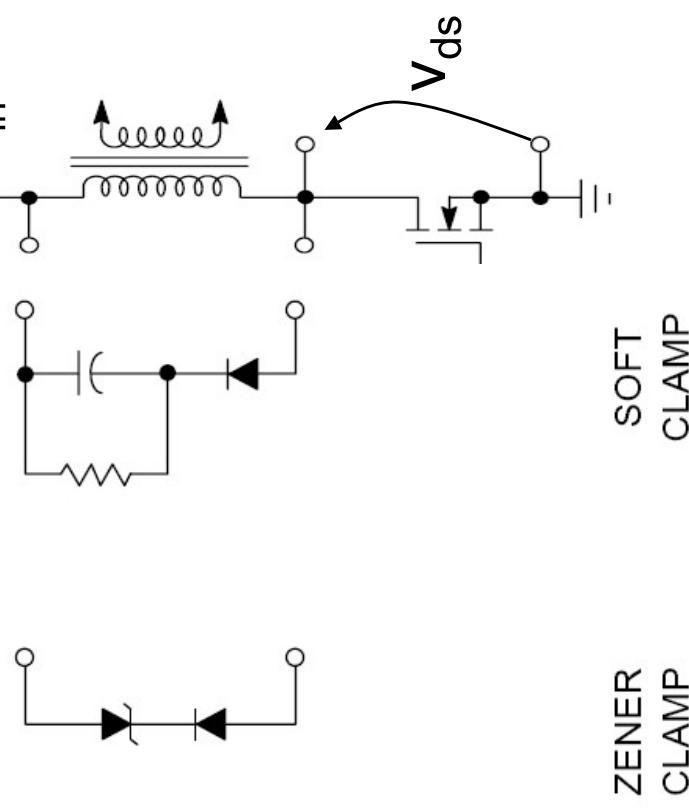

# Flyback regulator: leakage inductance

59

- Zener clamp

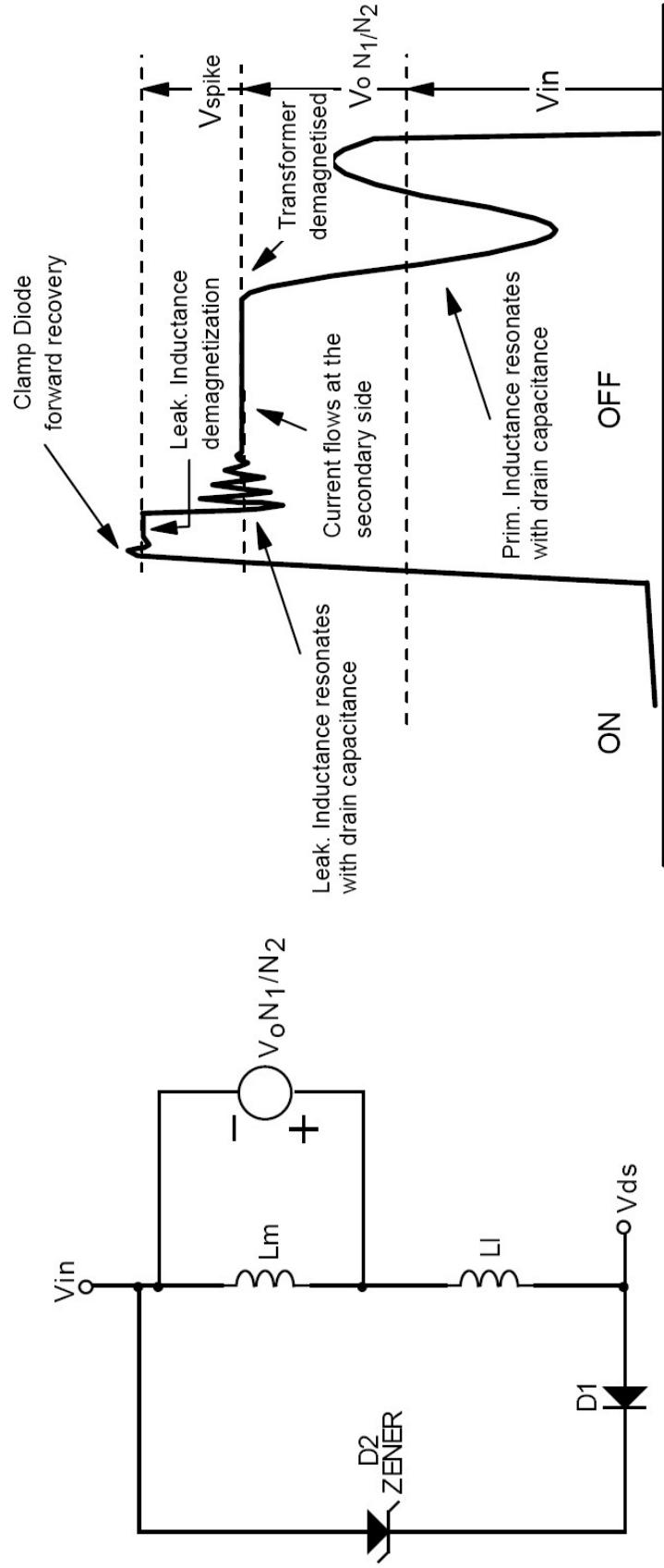

# Flyback regulator: leakage inductance

